









## GCE Electronics ET2 1142-01

Candidates' performance across questions

						
Question Title	N	Mean	S D	Max Mark	FF	Attempt %
1	883	5.1	1.5	6	85.5	99.1
2	857	3.4	2.1	6	56.5	96.2
3	883	4	2.4	7	56.7	99.1
4	870	3.5	2	6	59.1	97.6
5	868	4.8	2.5	8	59.9	97.4
6	843	3	1.7	5	60.7	94.6
7	839	3.4	2.5	8	42.9	94.2
8	862	3.3	1.7	7	47.1	96.8
9	831	3	2.5	7	42.4	93.3

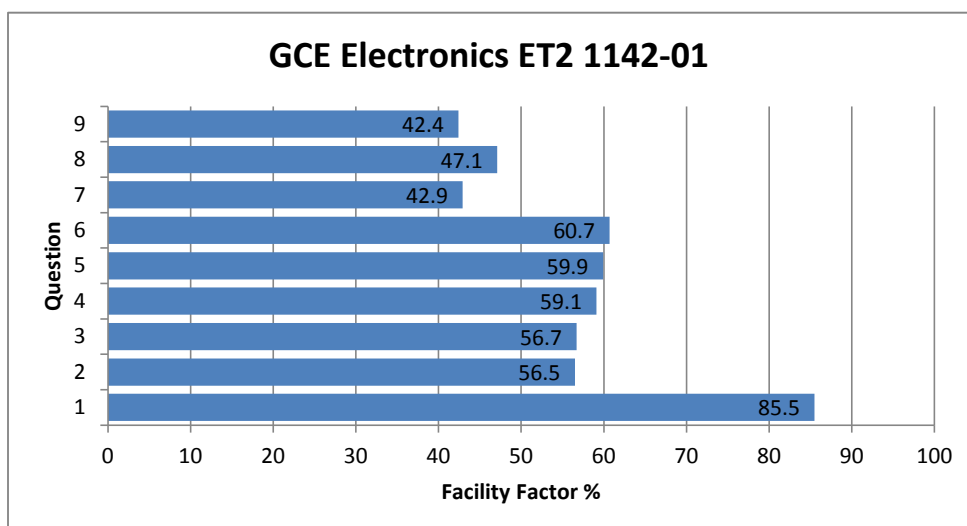

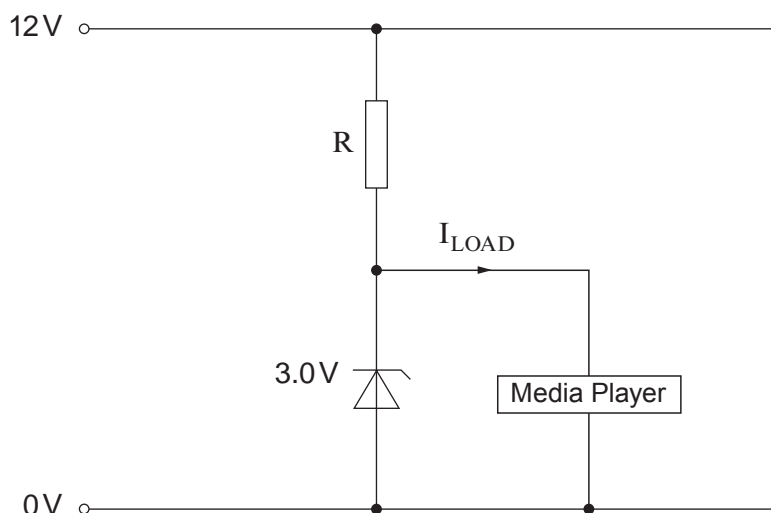7. A simple 3 V regulated power supply is required for a portable media player to be used with a 12 V car battery.



The zener diode requires a **minimum** current of 8 mA to maintain the zener voltage.

- (a) The power supply should be able to supply load currents up to 250 mA. Calculate the ideal value of resistor R.

[3]

.....

.....

.....

.....

- (b) Select the preferred value of resistor that you would use from the E24 series. Give a reason for your choice.

[1]

.....

.....

- (c) The output of the car battery varies, and can reach 14.5 V. The battery output is now 14.5 V. Calculate:

(i) the voltage across the zener diode; ..... [1]


(ii) the voltage across resistor R; ..... [1]

(iii) the power dissipated in resistor R. [2]

.....

.....

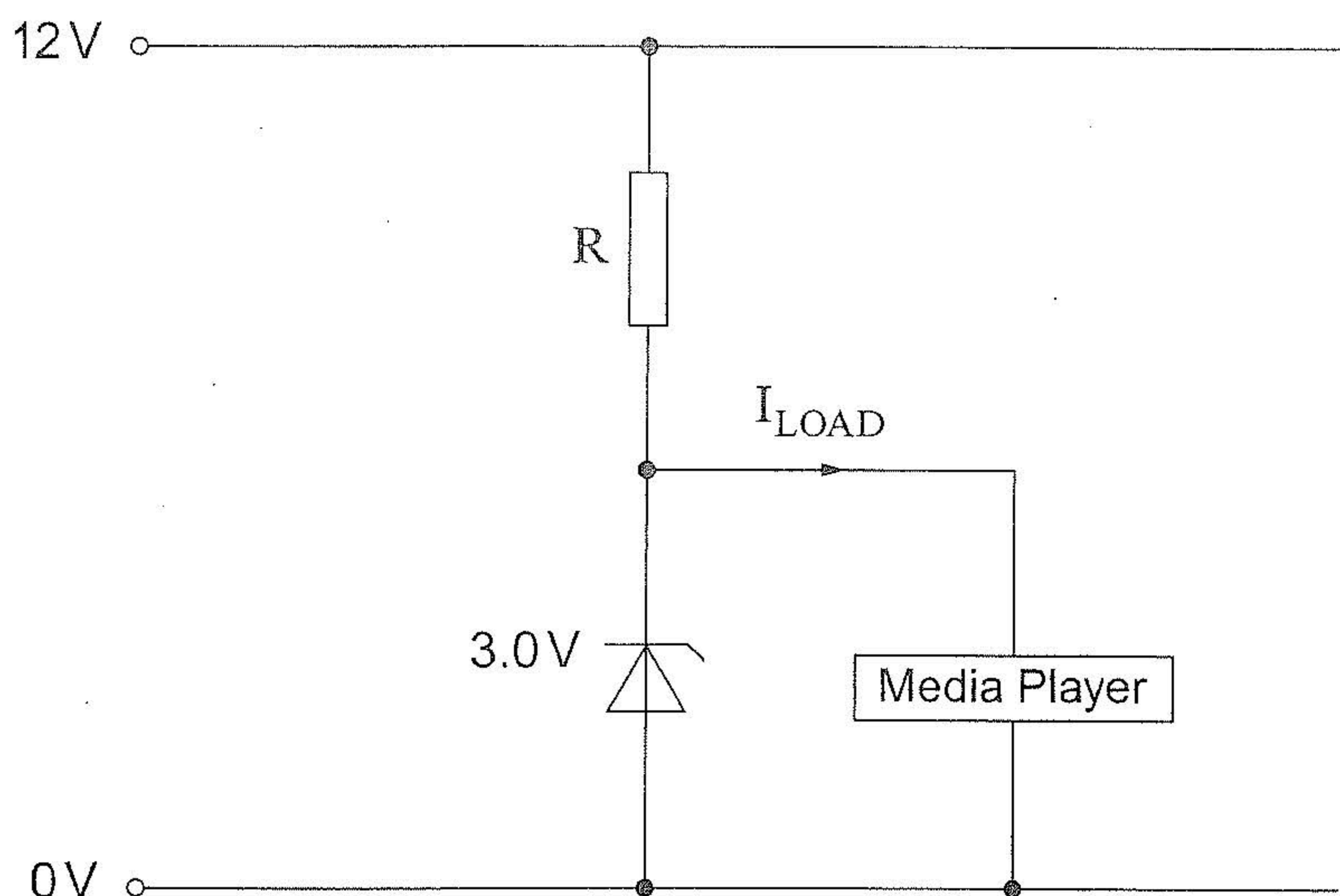7. A simple 3V regulated power supply is required for a portable media player to be used with a 12V car battery.



The zener diode requires a **minimum** current of 8 mA to maintain the zener voltage.

- (a) The power supply should be able to supply load currents up to 250 mA. Calculate the ideal value of resistor R.

[3]

$$258 \text{ mA} \checkmark \quad R = \frac{V}{I} \quad R = \frac{12}{258 \times 10^{-3}}$$

$$R = 46.5 \Omega \checkmark \text{ set}$$

- (b) Select the preferred value of resistor that you would use from the E24 series. Give a reason for your choice.

[1]

47  $\Omega$  because it's the closest to the ideal value

- (c) The output of the car battery varies, and can reach 14.5V. The battery output is now 14.5V. Calculate:

- (i) the voltage across the zener diode; 3V [1]


- (ii) the voltage across resistor R;  $14.5 - 3 = 11.5$  [1]

- (iii) the power dissipated in resistor R. [2]

$$P_R = IV = 0.25 \times 11.5 \quad I = 0.25 \text{ A}$$

$$P = 2.875 \text{ W}$$

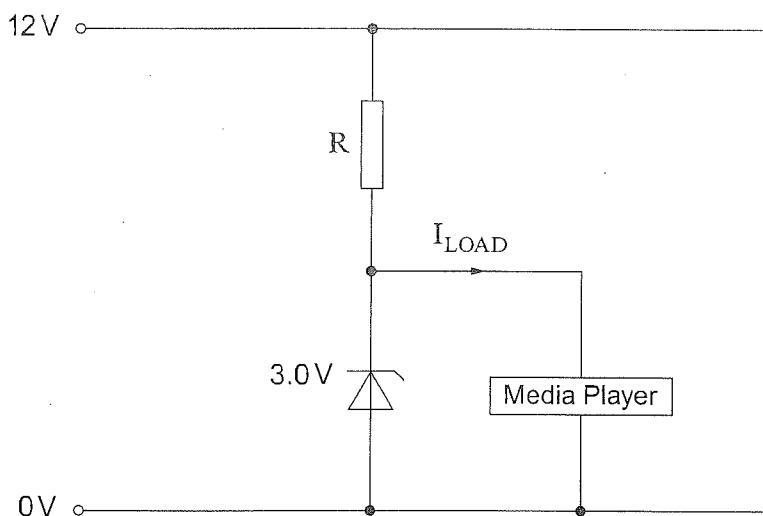7. A simple 3V regulated power supply is required for a portable media player to be used with a 12V car battery.



The zener diode requires a **minimum** current of 8mA to maintain the zener voltage.

- (a) The power supply should be able to supply load currents up to 250mA. Calculate the ideal value of resistor R.

[3]

\$2

$$258 \text{ mA} \checkmark$$

$$R = \frac{V}{I}$$

$$R = \frac{12}{258 \times 10^{-3}}$$



$$R = 46.5 \Omega \text{ set}$$

- (b) Select the preferred value of resistor that you would use from the E24 series. Give a reason for your choice.

[1]

0

47Ω because it's the closest to the ideal value X



- (c) The output of the car battery varies, and can reach 14.5V. The battery output is now 14.5V. Calculate:

(i) the voltage across the zener diode;  $3\text{V} \checkmark$  [1] 1

(ii) the voltage across resistor R;  $V = I \times R = 14.5 - 3 = 11.5\text{V}$  [1] 1

(iii) the power dissipated in resistor R. [2] 2

$$P_R = IV = 0.25 \times 11.5 \quad I = 11.5$$


$$P = 2.875 \text{ W set}$$

$$I = \frac{47 \text{ set}}{0.25 \text{ A}}$$

8/6



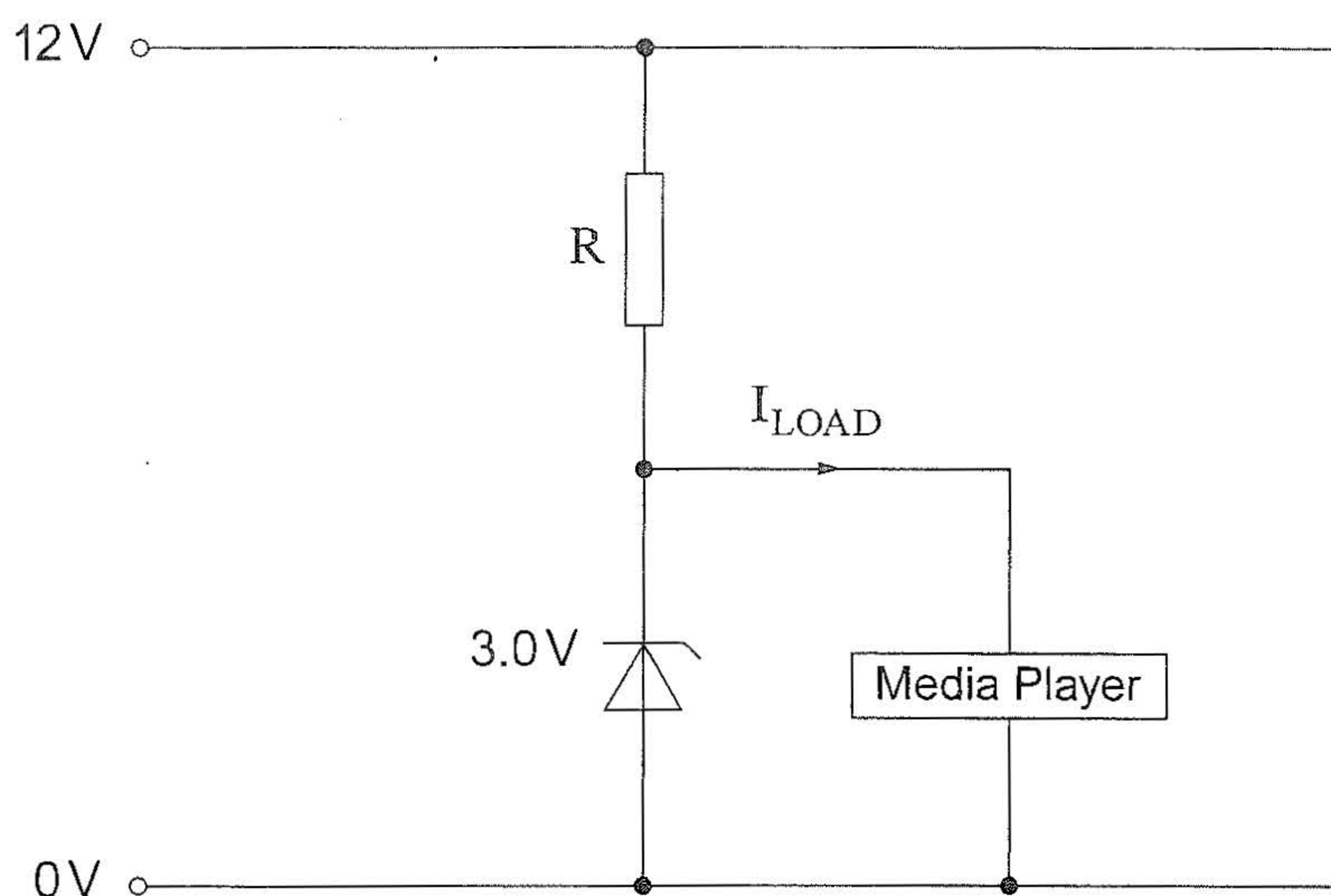7. A simple 3V regulated power supply is required for a portable media player to be used with a 12V car battery.



The zener diode requires a **minimum** current of 8 mA to maintain the zener voltage.

- (a) The power supply should be able to supply load currents up to 250 mA. Calculate the ideal value of resistor R.

[3]

$$250 + 8 = 258 \text{ mA}$$

$$12 - 3 = 9$$

$$9 \div 0.258 = 34.9$$

- (b) Select the preferred value of resistor that you would use from the E24 series. Give a reason for your choice.

[1]

33Ω because otherwise it could not support up to 250 mA

- (c) The output of the car battery varies, and can reach 14.5V. The battery output is now 14.5V. Calculate:


(i) the voltage across the zener diode; 3.625 [1]

(ii) the voltage across resistor R; 10.875 [1]

(iii) the power dissipated in resistor R. ecf. [2]

$$10.875 \div 33 \Omega \times 10.875 = 3.58 \text{ W}$$

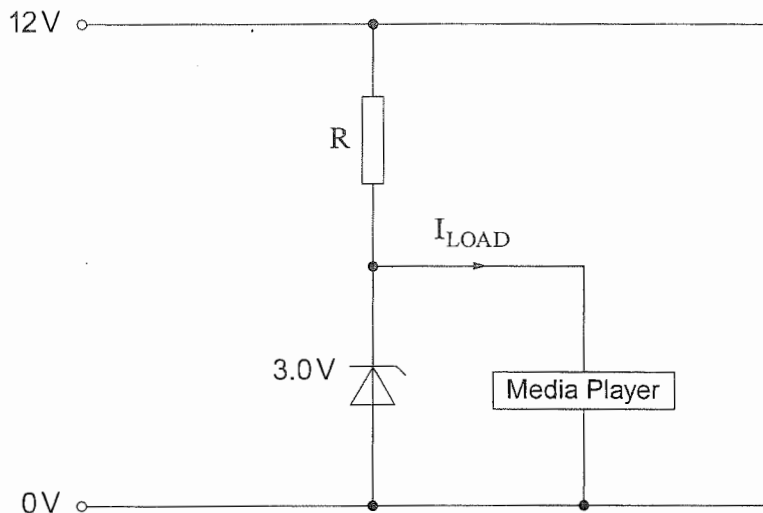7. A simple 3V regulated power supply is required for a portable media player to be used with a 12V car battery.



The zener diode requires a **minimum** current of 8 mA to maintain the zener voltage.

- (a) The power supply should be able to supply load currents up to 250 mA. Calculate the ideal value of resistor R.

[3]

$$250 + 8 = 258 \text{ mA} \checkmark$$

$$12 - 3 = 9 \checkmark$$

$$9 \div 0.258 = 34.9 \checkmark$$

3

- (b) Select the preferred value of resistor that you would use from the E24 series. Give a reason for your choice.

[1]

33Ω because otherwise it could not support up to 250 mA ✓

1

- (c) The output of the car battery varies, and can reach 14.5V. The battery output is now 14.5V. Calculate:

(i) the voltage across the zener diode; 3.625 [1] 0

(ii) the voltage across resistor R; 10.875 [1] 0


(iii) the power dissipated in resistor R. ecf. [2] 2

$$10.875 \times 0.258 = 2.806 \text{ W} \checkmark$$

6



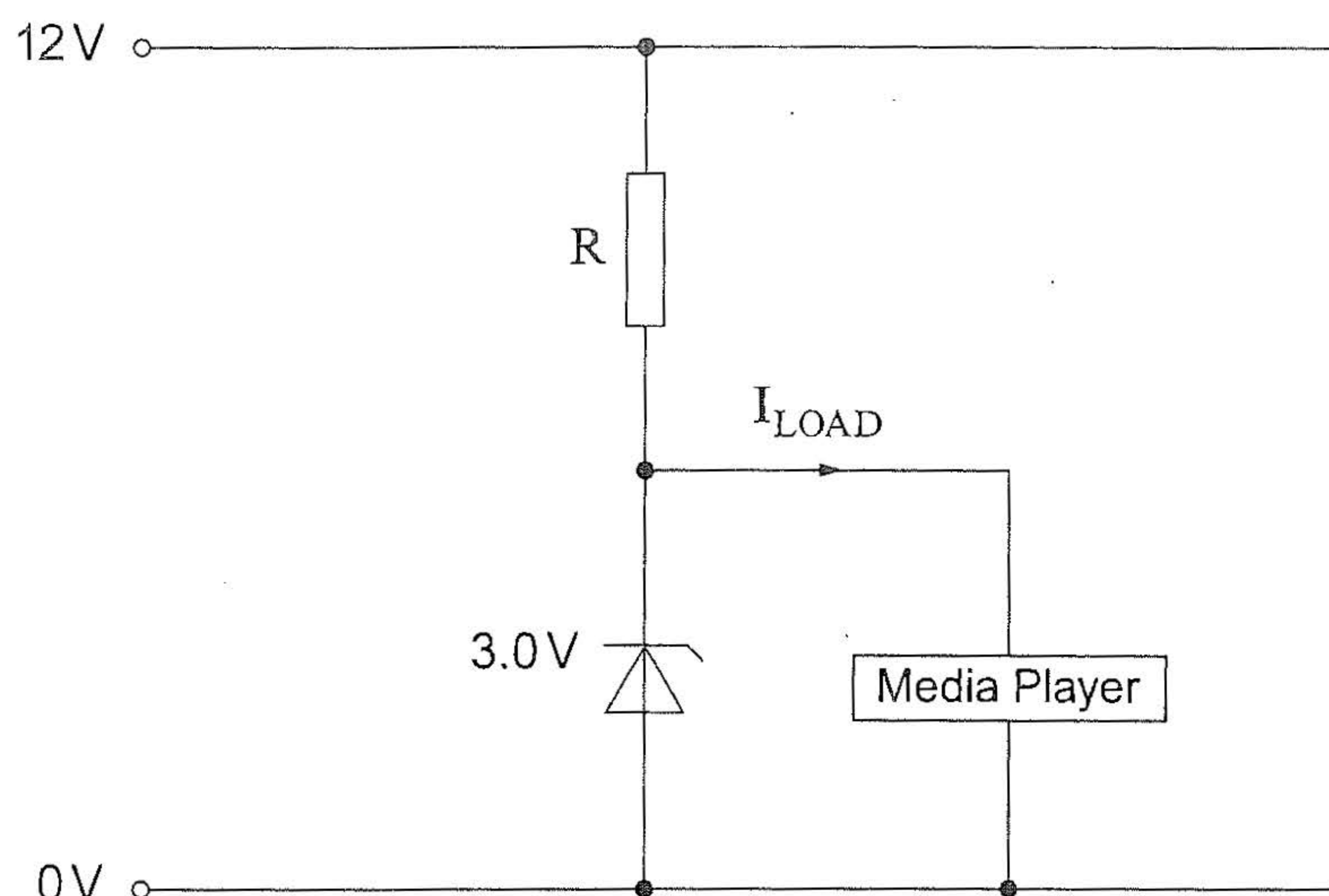7. A simple 3V regulated power supply is required for a portable media player to be used with a 12V car battery.



The zener diode requires a **minimum** current of 8 mA to maintain the zener voltage.

- (a) The power supply should be able to supply load currents up to 250 mA. Calculate the ideal value of resistor R.

[3]

$$\begin{aligned}
 &\frac{12}{8 \times 10^{-3}} = 1500 \quad 12 - 0.7 = 11.3 \text{ V} \\
 &\frac{11.3}{8 \times 10^{-3}} = 1412.5 \quad 250 + 8 = 258 \text{ mA} \\
 &\frac{11.3}{250 \times 10^{-3}} = 45.2 \quad \frac{11.3}{258 \times 10^{-3}} = 43.798 \\
 &\quad \quad \quad = 43.8 \Omega
 \end{aligned}$$

- (b) Select the preferred value of resistor that you would use from the E24 series. Give a reason for your choice.

[1]

43Ω so it can give more so it doesn't cut out

- (c) The output of the car battery varies, and can reach 14.5 V. The battery output is now 14.5 V. Calculate:


(i) the voltage across the zener diode; 3.625 [1]

(ii) the voltage across resistor R; 10.875 [1]

(iii) the power dissipated in resistor R. [2]

$$\begin{aligned}
 P &= VI \quad V = 10.875 \quad P = 3.67 \\
 I &= 0.34
 \end{aligned}$$

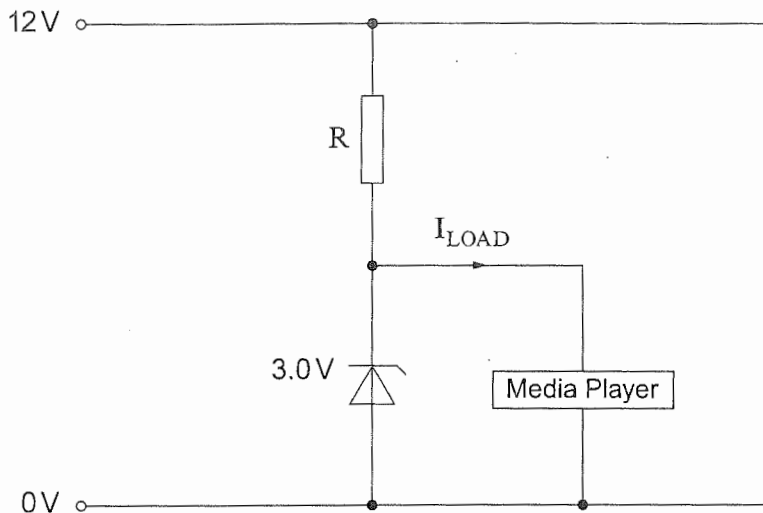7. A simple 3V regulated power supply is required for a portable media player to be used with a 12V car battery.



The zener diode requires a **minimum** current of 8 mA to maintain the zener voltage.

- (a) The power supply should be able to supply load currents up to 250 mA. Calculate the ideal value of resistor R.

[3]

2

$$\begin{aligned}
 &12 - 0.7 = 11.3 \text{ V} \\
 &11.3 - 3 = 8.3 \text{ V} \\
 &8.3 \text{ V} / 0.25 \text{ A} = 33.2 \Omega \\
 &11.3 \text{ V} - 3 \text{ V} = 8.3 \text{ V} \\
 &8.3 \text{ V} / 0.25 \text{ A} = 33.2 \Omega \\
 &11.3 \text{ V} - 3 \text{ V} = 8.3 \text{ V} \\
 &8.3 \text{ V} / 0.25 \text{ A} = 33.2 \Omega
 \end{aligned}$$

- (b) Select the preferred value of resistor that you would use from the E24 series. Give a reason for your choice.

[1]

1

43Ω so it can give more so it doesn't cut out

- (c) The output of the car battery varies, and can reach 14.5V. The battery output is now 14.5V. Calculate:

(i) the voltage across the zener diode; 3.625 [1]

(ii) the voltage across resistor R; 10.875 [1]


(iii) the power dissipated in resistor R. [2]

$$\begin{aligned}
 P &= VI \\
 V &= 10.875 \\
 I &= 0.34 \text{ A} \\
 P &= 3.67 \text{ W}
 \end{aligned}$$

3




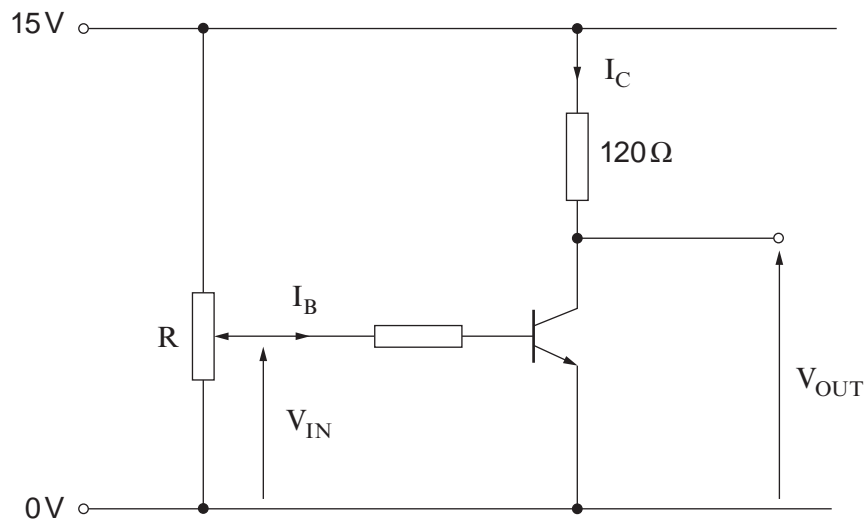8. The following circuit is set up to investigate a transistor switching circuit.



Potentiometer  $R$  is varied and readings of  $V_{IN}$ ,  $V_{OUT}$ ,  $I_B$  and  $I_C$  are taken.

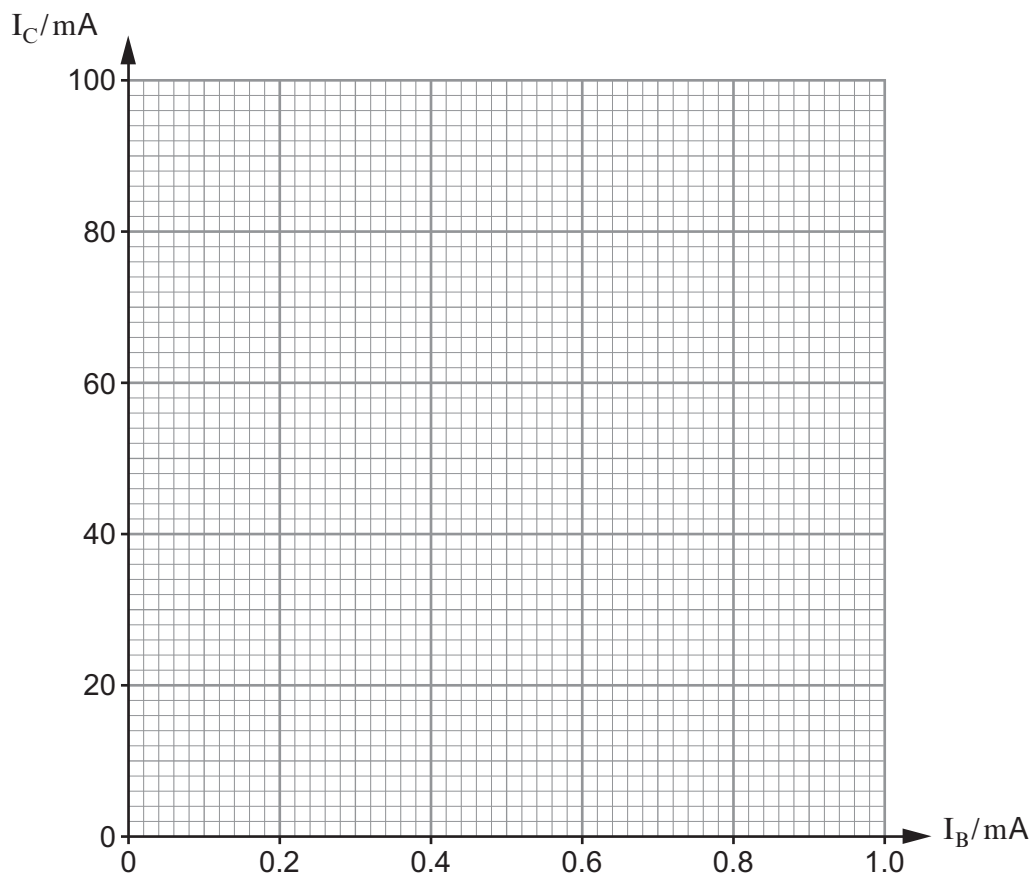- (a) As the base current is increased from 0.2 to 0.8 mA the collector current increases from 16 to 64 mA and the transistor does not saturate.
- (i) Complete the graph below to show how the ammeter readings change as  $I_B$  is increased from 0 to 1 mA. The transistor does not saturate. [1]




(ii) Determine the current gain ( $h_{FE}$ ) of the transistor.

[1]

.....

.....

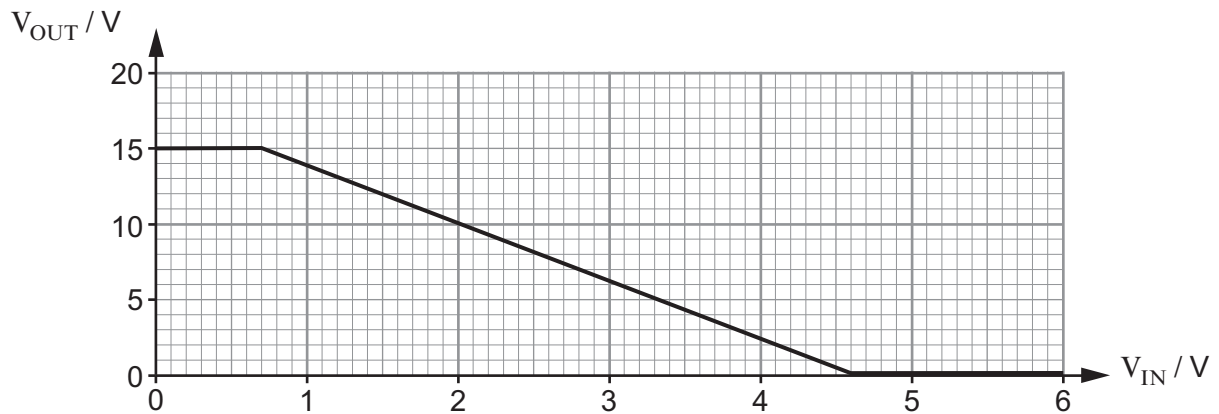(b) A second graph was drawn to show how  $V_{OUT}$  changed as  $V_{IN}$  was increased from 0 to 6 V.



Use the graph to determine:

(i) the minimum value of  $V_{IN}$  required to saturate the transistor;

[1]

.....

(ii) the value of  $V_{OUT}$ , when  $V_{IN} = 3.1 V$ .

[1]

.....

(c)  $V_{IN} = 3.1 V$  and the load resistor =  $120 \Omega$ .

Calculate the collector current and the power dissipated in the transistor.

[3]

.....

.....


.....

.....

.....


**TURN OVER FOR THE LAST QUESTION.**

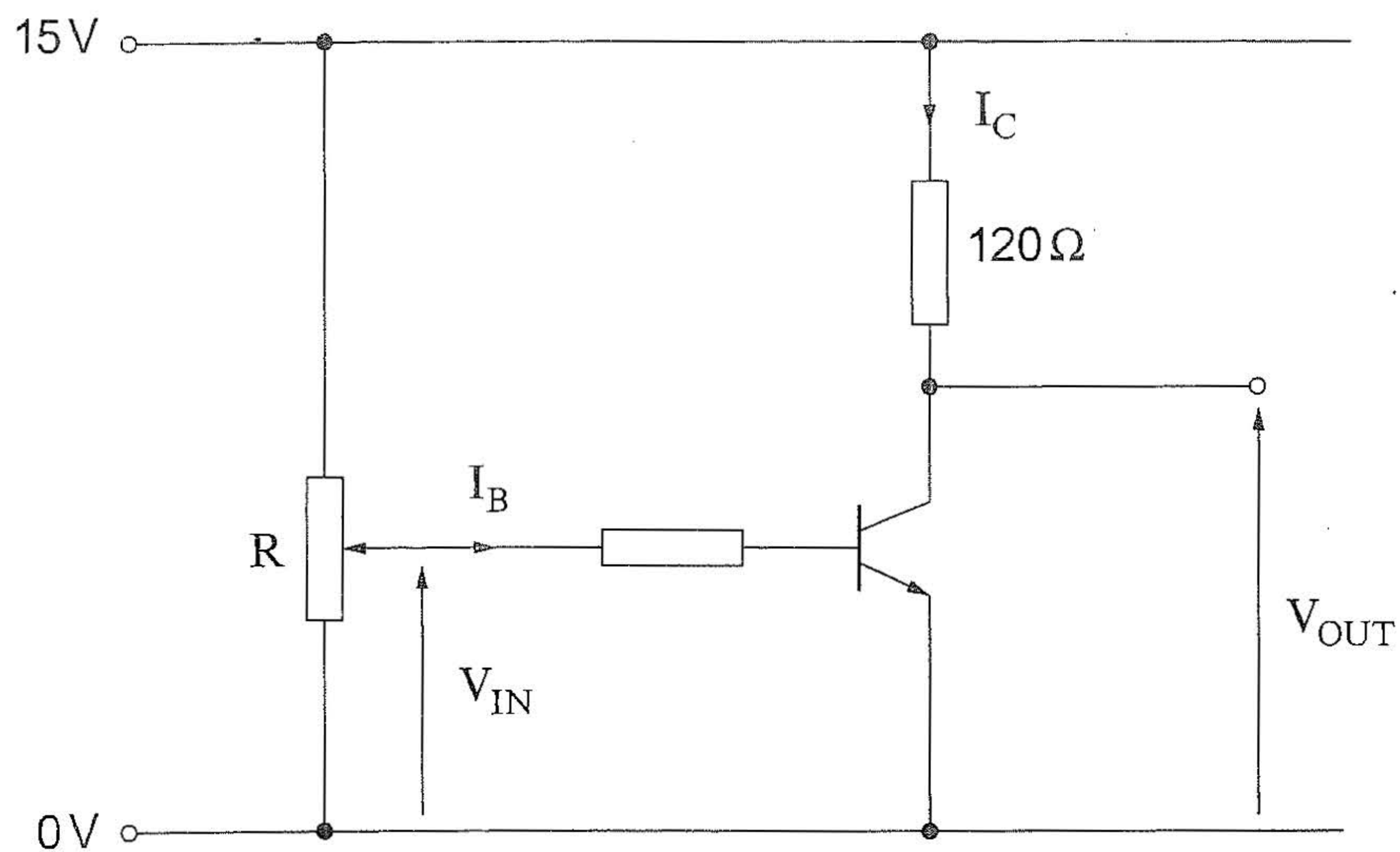8. The following circuit is set up to investigate a transistor switching circuit.



Potentiometer R is varied and readings of  $V_{IN}$ ,  $V_{OUT}$ ,  $I_B$  and  $I_C$  are taken.

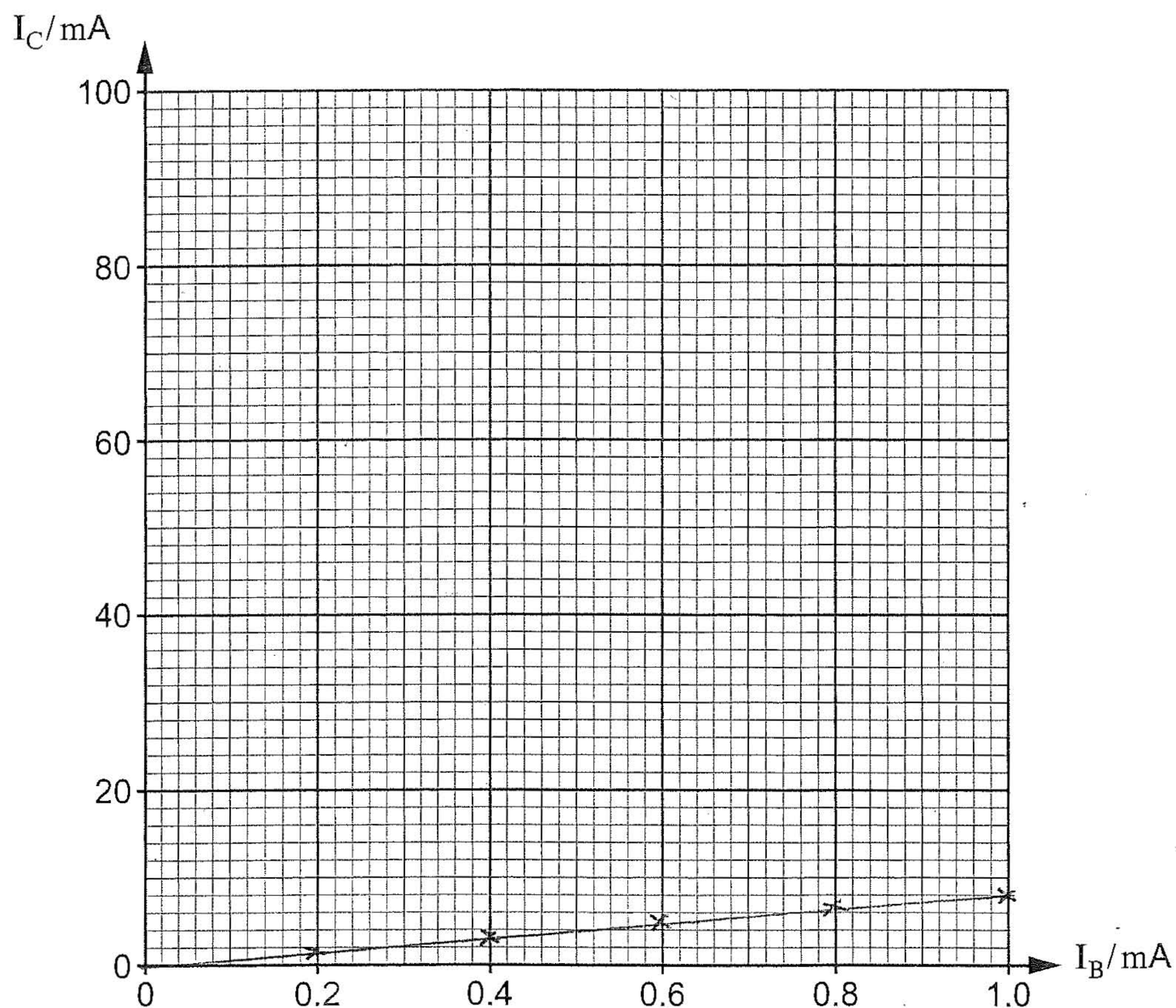- (a) As the base current is increased from 0.2 to 0.8 mA the collector current increases from 16 to 64 mA and the transistor does not saturate.
- (i) Complete the graph below to show how the ammeter readings change as  $I_B$  is increased from 0 to 1 mA. The transistor does not saturate. [1]






- (ii) Determine the current gain ( $h_{FE}$ ) of the transistor.

[1]

$$\frac{0.8}{0.2} = 4$$

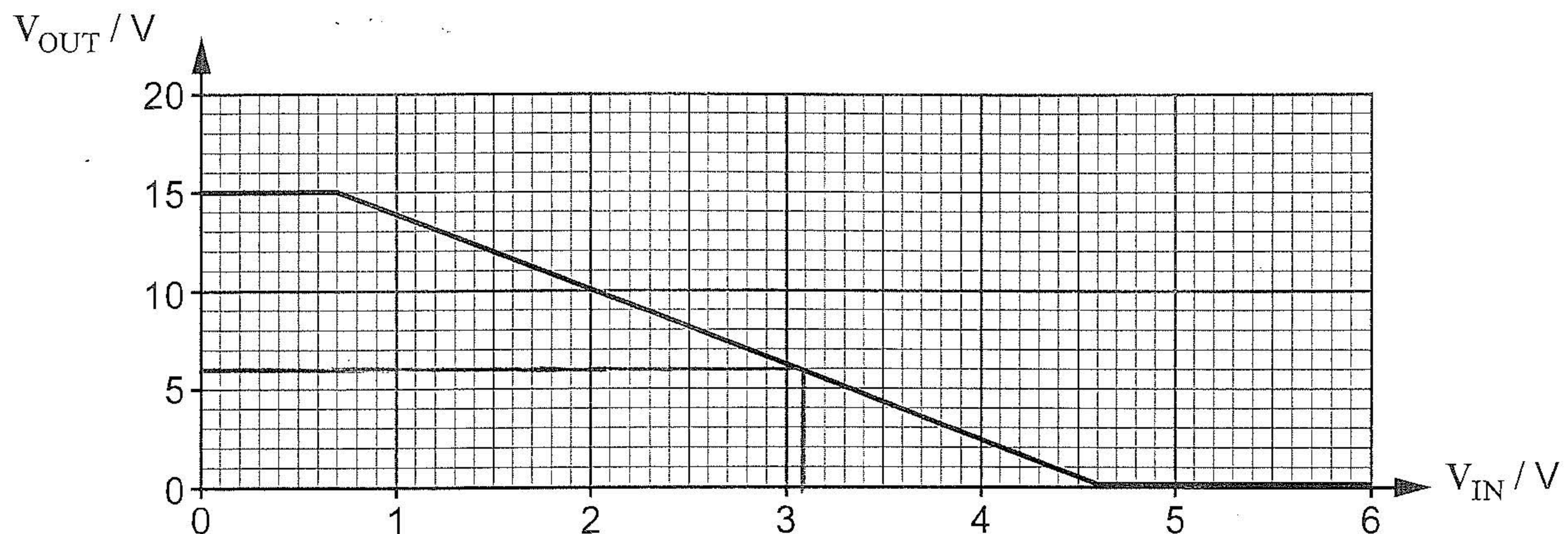- (b) A second graph was drawn to show how  $V_{OUT}$  changed as  $V_{IN}$  was increased from 0 to 6 V.



Use the graph to determine:

- (i) the minimum value of  $V_{IN}$  required to saturate the transistor;

4.6V

[1]

- (ii) the value of  $V_{OUT}$  when  $V_{IN} = 3.1V$ .

6V

[1]

- (c)  $V_{IN} = 3.1V$  and the load resistor =  $120\Omega$ .

Calculate the collector current and the power dissipated in the transistor.

[3]


$$3.1V \quad \text{let } 6 \div 120 = 0.05A$$

$$P = IV$$

$$0.05 \times 6 = 0.3W$$


**TURN OVER FOR THE LAST QUESTION.**

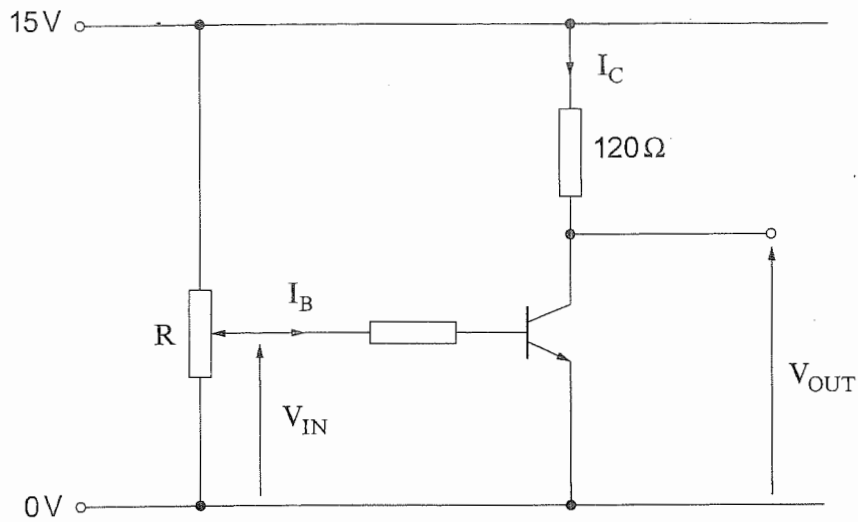8. The following circuit is set up to investigate a transistor switching circuit.



Potentiometer  $R$  is varied and readings of  $V_{IN}$ ,  $V_{OUT}$ ,  $I_B$  and  $I_C$  are taken.

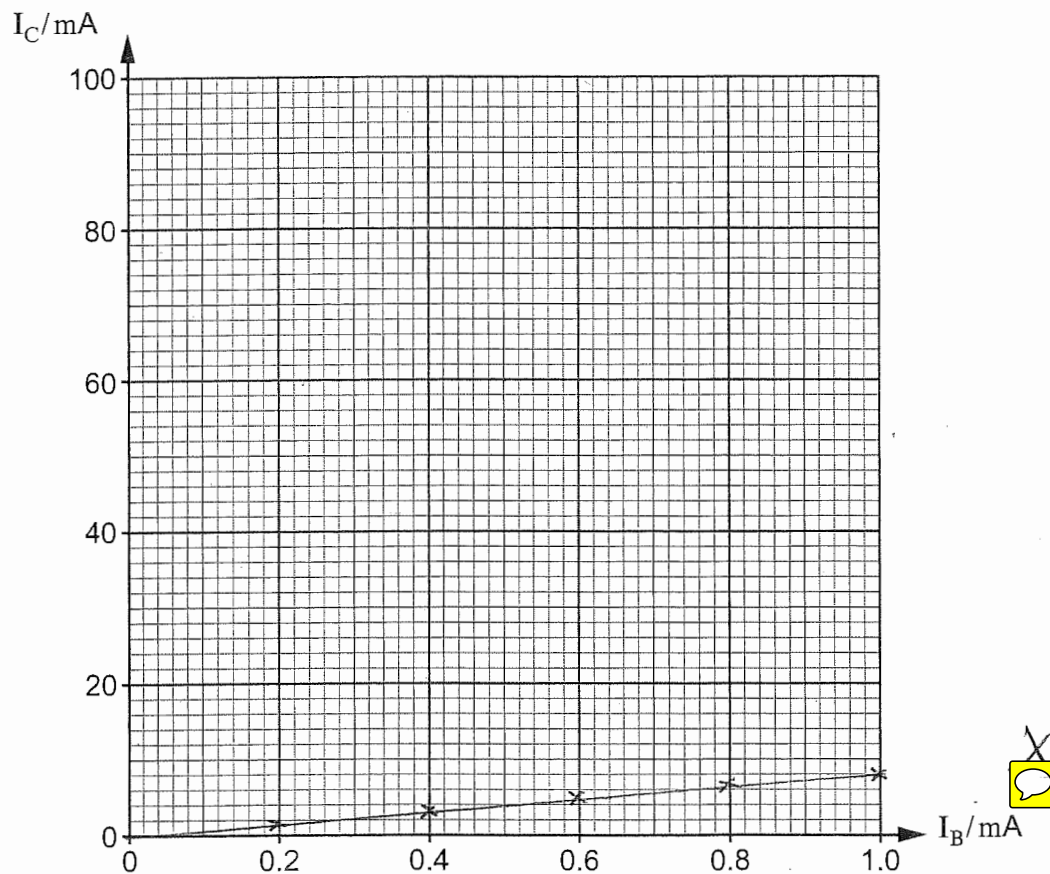- (a) As the base current is increased from 0.2 to 0.8 mA the collector current increases from 16 to 64 mA and the transistor does not saturate.
- (i) Complete the graph below to show how the ammeter readings change as  $I_B$  is increased from 0 to 1 mA. The transistor does not saturate. [1]




- (ii) Determine the current gain ( $h_{FE}$ ) of the transistor.

Examiner  
only  
[1]

$$\frac{0.8}{0.2} = 4 \quad \times$$

0

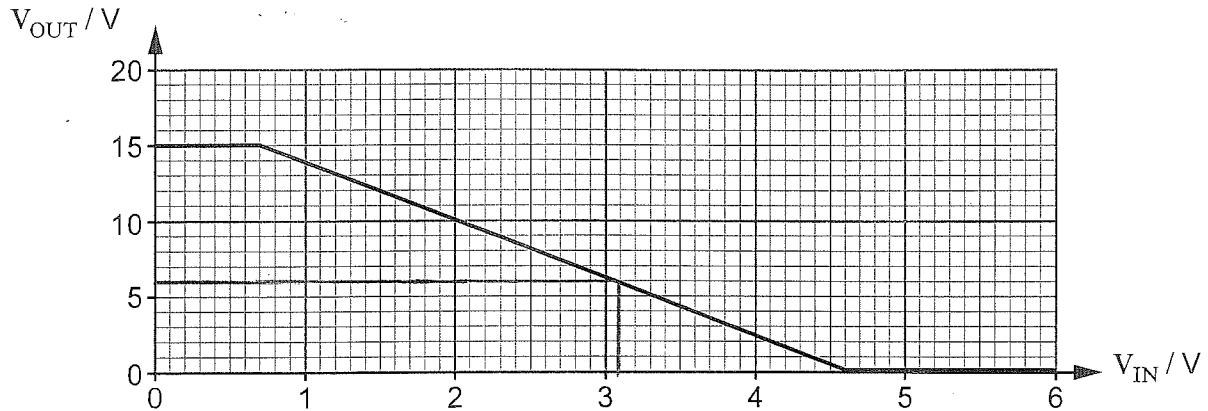- (b) A second graph was drawn to show how  $V_{OUT}$  changed as  $V_{IN}$  was increased from 0 to 6 V.



Use the graph to determine:

- (i) the minimum value of  $V_{IN}$  required to saturate the transistor;

4.6V ✓

[1]

- (ii) the value of  $V_{OUT}$  when  $V_{IN} = 3.1$  V.

6V ✓

[1]

- (c)  $V_{IN} = 3.1$  V and the load resistor =  $120 \Omega$ .

Calculate the collector current and the power dissipated in the transistor.

[3]

$$3.1 \times \frac{6}{120} = 0.155 \text{ A}$$

$$P = 1 \times V$$

$$0.05 \times 6 = 0.3 \text{ W}$$


2

4

**TURN OVER FOR THE LAST QUESTION.**




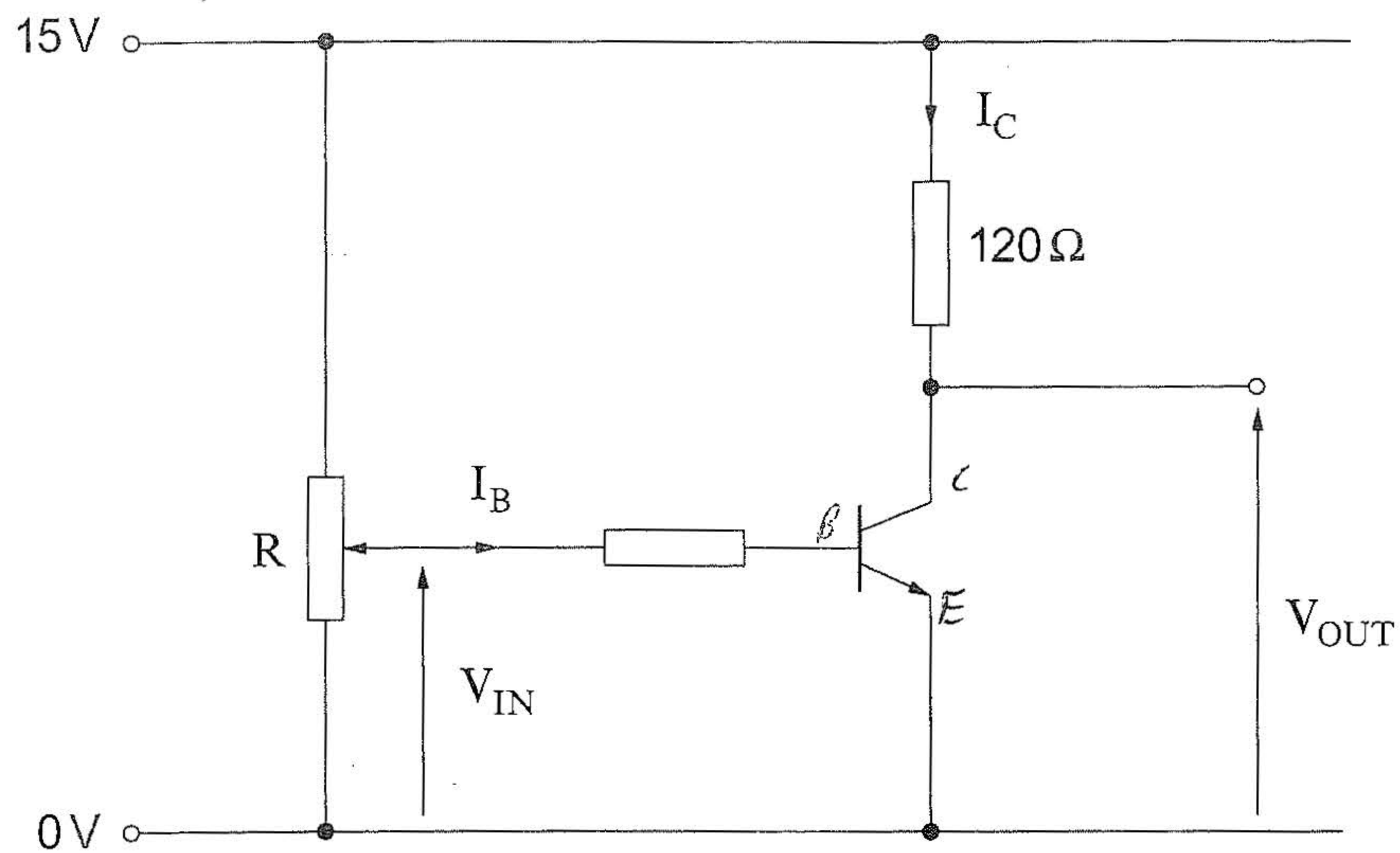8. The following circuit is set up to investigate a transistor switching circuit.



Potentiometer R is varied and readings of  $V_{IN}$ ,  $V_{OUT}$ ,  $I_B$  and  $I_C$  are taken.

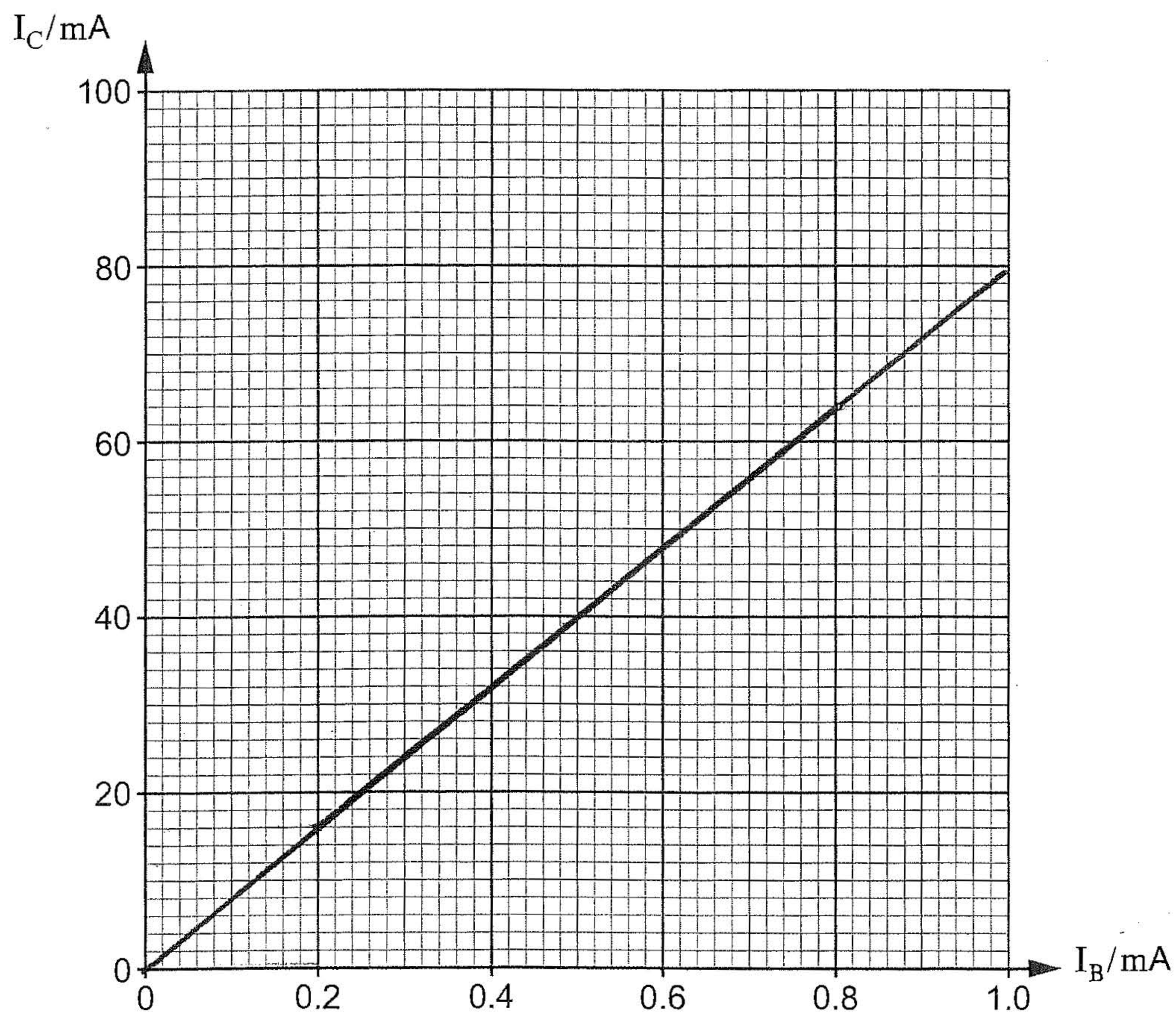- (a) As the base current is increased from 0.2 to 0.8 mA the collector current increases from 16 to 64 mA and the transistor does not saturate.
- (i) Complete the graph below to show how the ammeter readings change as  $I_B$  is increased from 0 to 1 mA. The transistor does not saturate. [1]






- (ii) Determine the current gain ( $h_{FE}$ ) of the transistor. [1]

$$h_{FE} = \frac{I_c}{I_b} = \frac{64}{0.8 \times 10^{-3}} = 80 \times 10^3$$

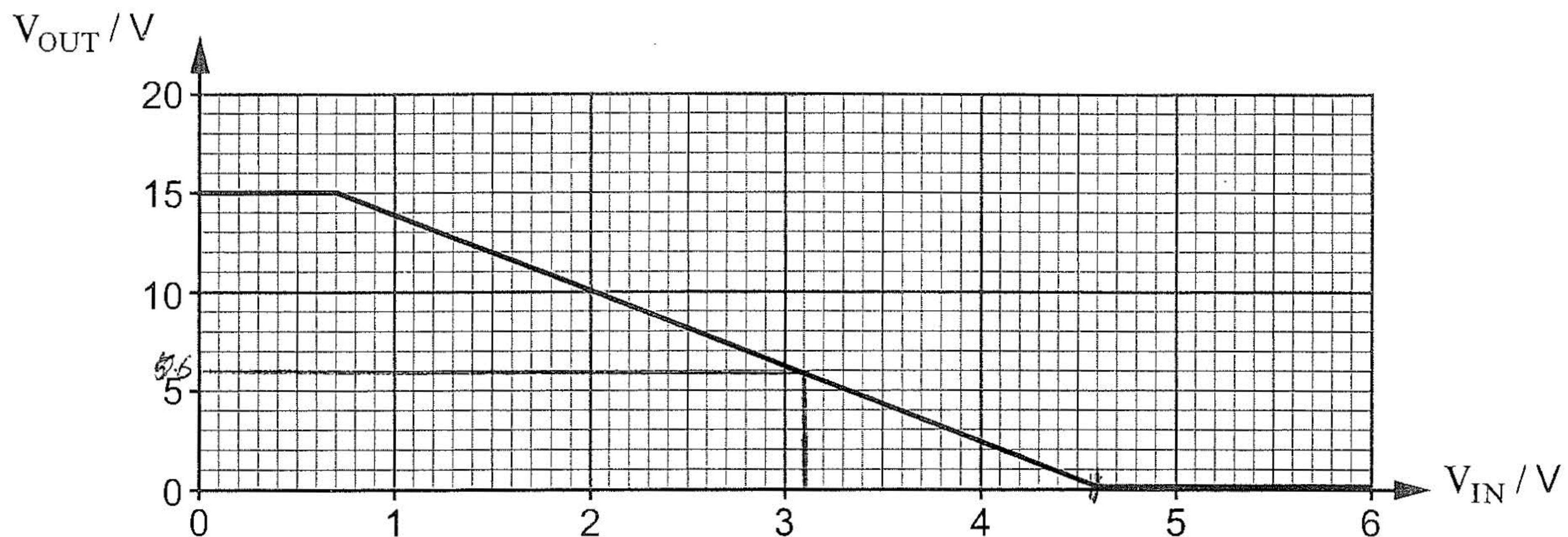- (b) A second graph was drawn to show how  $V_{OUT}$  changed as  $V_{IN}$  was increased from 0 to 6 V.



Use the graph to determine:

- (i) the minimum value of  $V_{IN}$  required to saturate the transistor;

4.6 V

[1]

- (ii) the value of  $V_{OUT}$ , when  $V_{IN} = 3.1$  V.

6 V

[1]

- (c)  $V_{IN} = 3.1$  V and the load resistor =  $120 \Omega$ .

Calculate the collector current and the power dissipated in the transistor. [3]


$$\frac{15}{120} = 0.125 = I_c$$

$$P = V \times I \quad 3.1 \times 0.125 = 0.3875$$

$$\approx 0.39 \text{ W}$$


**TURN OVER FOR THE LAST QUESTION.**

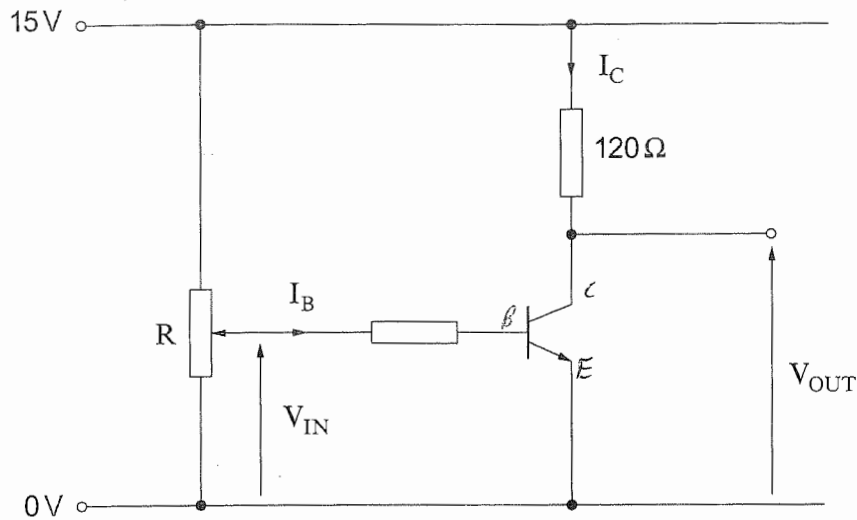8. The following circuit is set up to investigate a transistor switching circuit.



Potentiometer R is varied and readings of  $V_{IN}$ ,  $V_{OUT}$ ,  $I_B$  and  $I_C$  are taken.

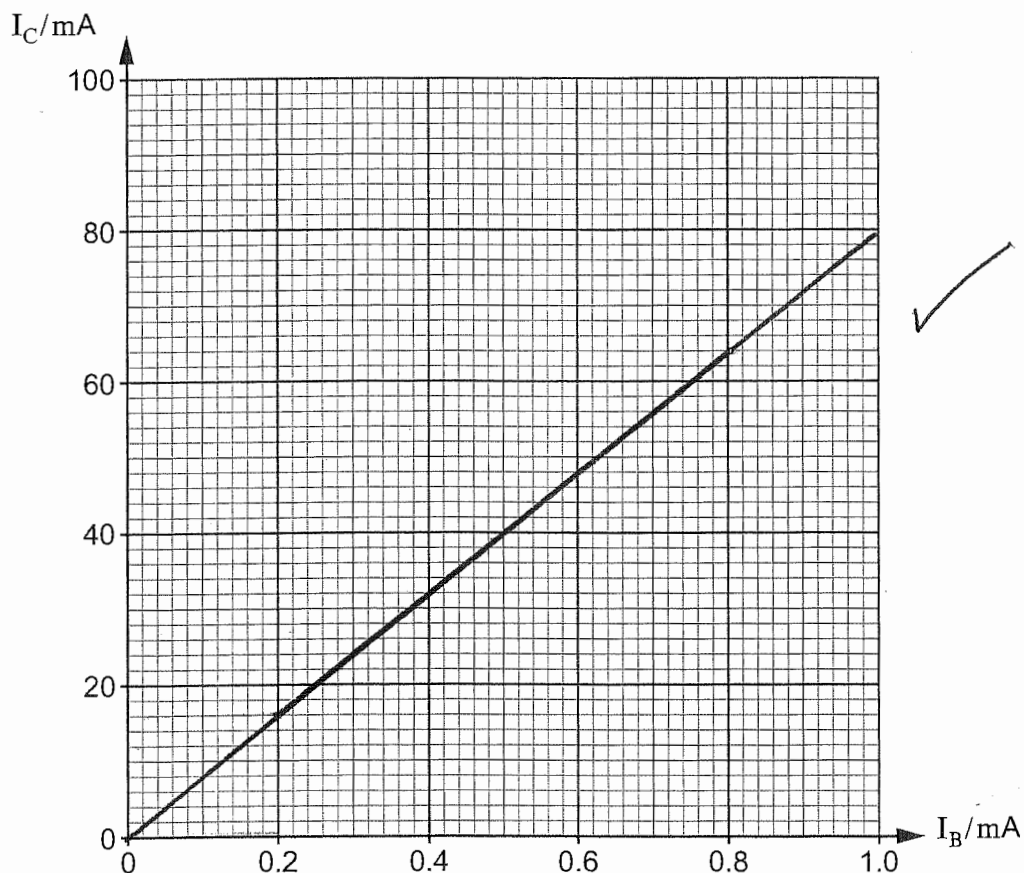- (a) As the base current is increased from 0.2 to 0.8 mA the collector current increases from 16 to 64 mA and the transistor does not saturate.
- (i) Complete the graph below to show how the ammeter readings change as  $I_B$  is increased from 0 to 1 mA. The transistor does not saturate. [1]






(ii) Determine the current gain ( $h_{FE}$ ) of the transistor.

[1]

Examiner only

$$h_{FE} = \frac{I_c}{I_b} = \frac{64}{0.8 \times 10^{-3}} = 80 \times 10^3 \checkmark$$

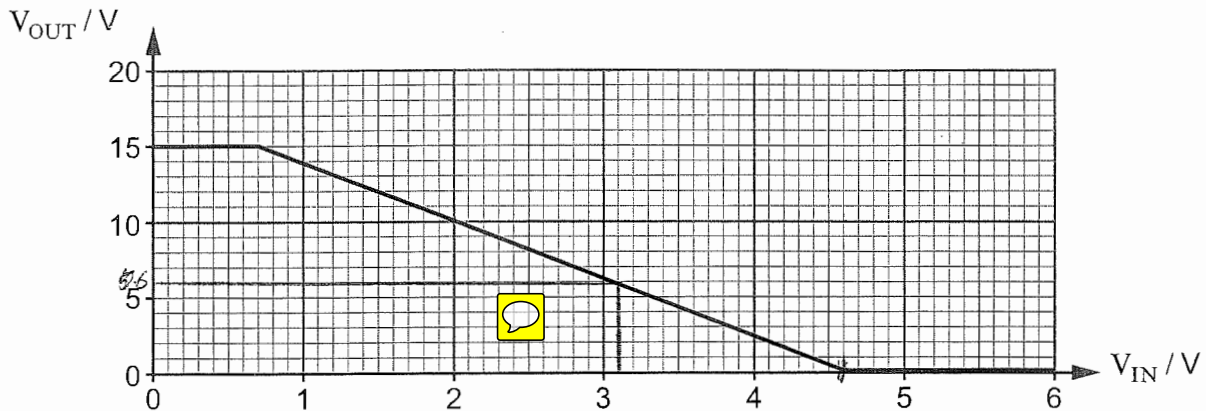(b) A second graph was drawn to show how  $V_{OUT}$  changed as  $V_{IN}$  was increased from 0 to 6V.



Use the graph to determine:

(i) the minimum value of  $V_{IN}$  required to saturate the transistor;

4.6V ✓

[1]

(ii) the value of  $V_{UT}$  when  $V_{IN} = 3.1V$ .

6V ✓

[1]

(c)  $V_{IN} = 3.1V$  and the load resistor =  $120\Omega$ .

Calculate the collector current and the power dissipated in the transistor.


[3]

$$\frac{15}{120} = 0.125 = I_c$$

$$P = V \times I \quad 3.1 \times 0.125 = 0.3875$$


$$\approx 0.39W$$

**TURN OVER FOR THE LAST QUESTION.**

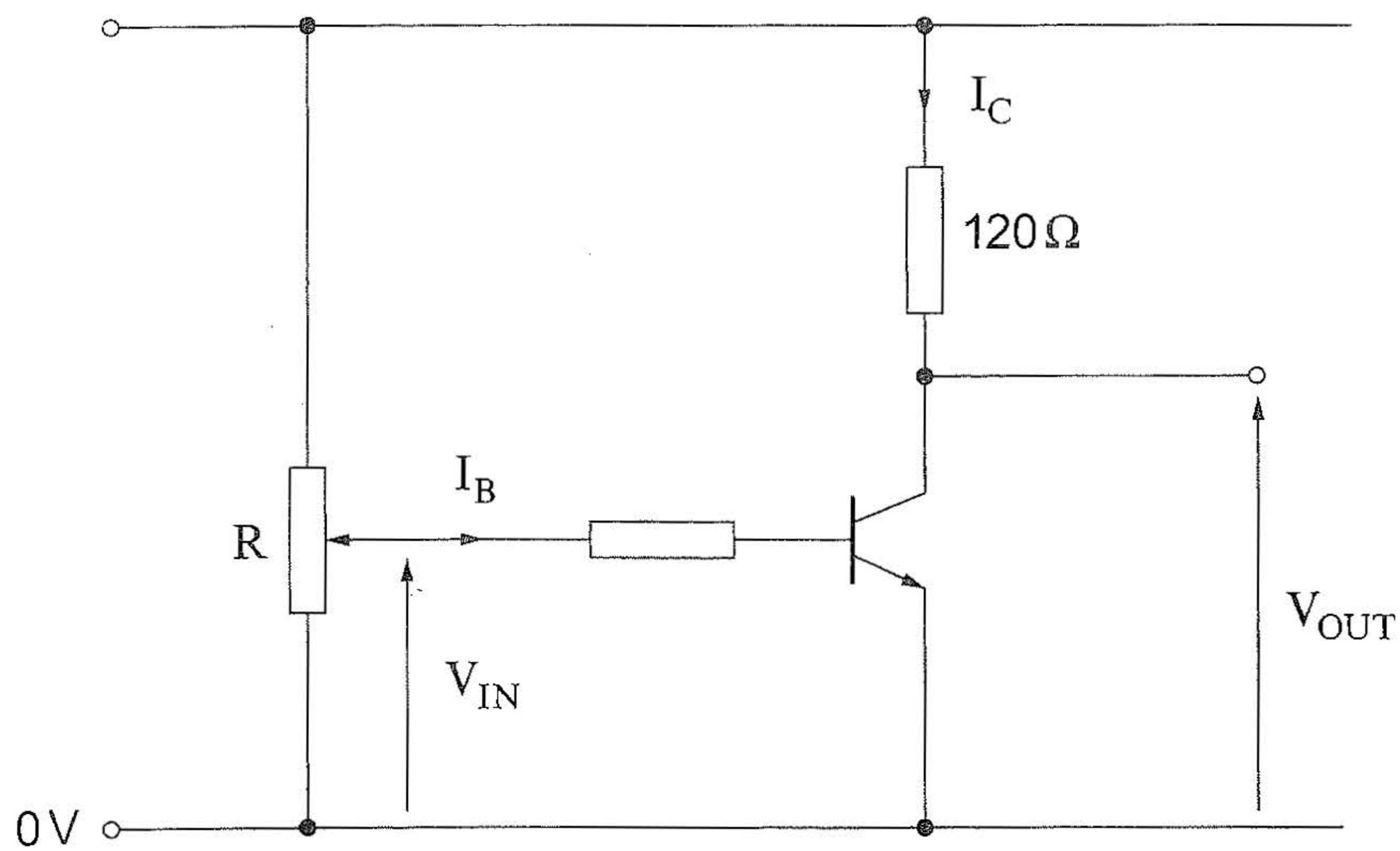

Potentiometer R is varied and readings of  $V_{IN}$ ,  $V_{OUT}$ ,  $I_B$  and  $I_C$  are taken.

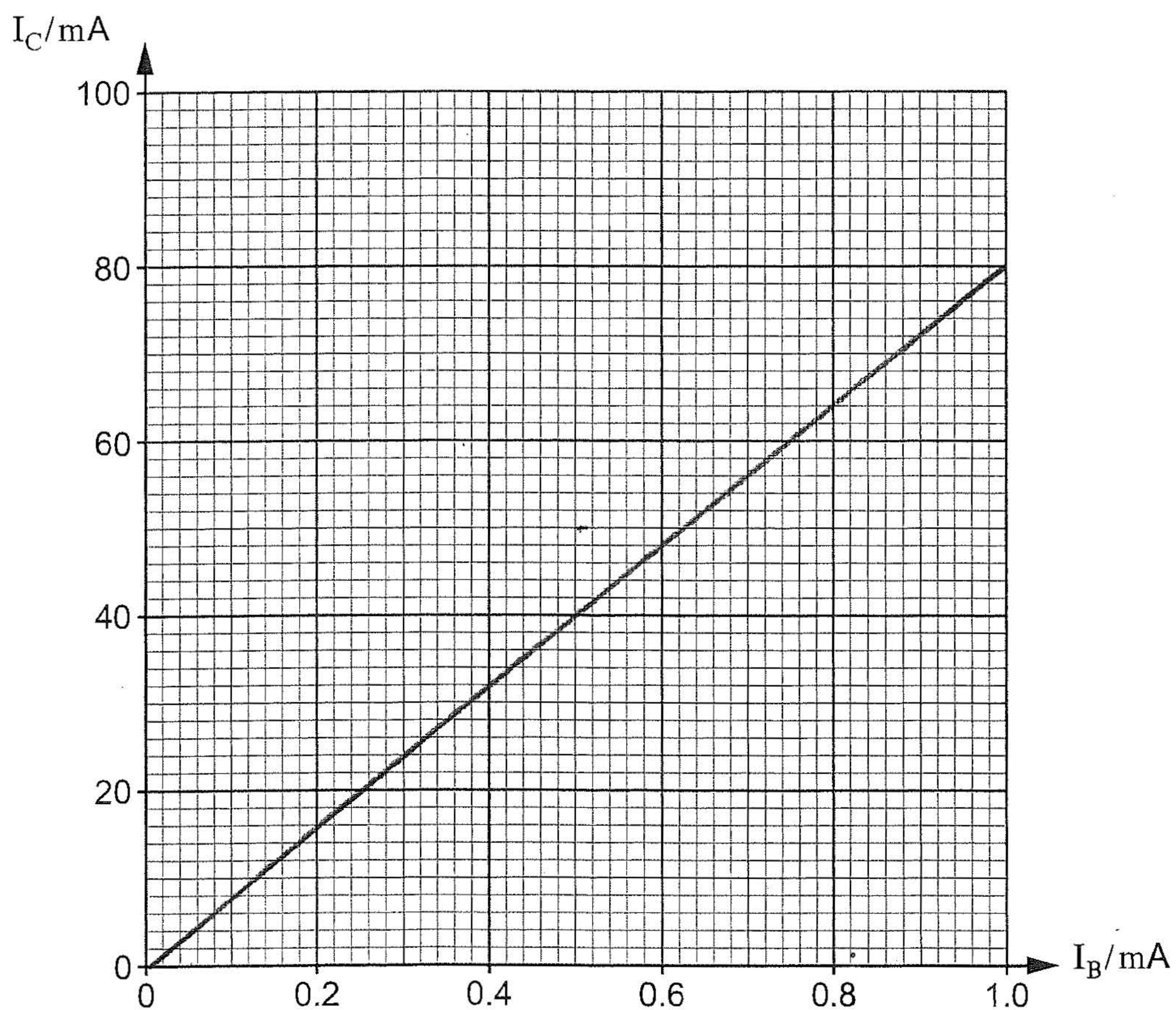- (a) As the base current is increased from 0.2 to 0.8 mA the collector current increases from 16 to 64 mA and the transistor does not saturate.
- (i) Complete the graph below to show how the ammeter readings change as  $I_B$  is increased from 0 to 1 mA. The transistor does not saturate. [1]






- (ii) Determine the current gain ( $h_{FE}$ ) of the transistor. [1]

$$h_{FE} = \frac{I_C}{I_B} = \frac{0.8 \text{ mA}}{64 \text{ mA}} = 0.0125$$

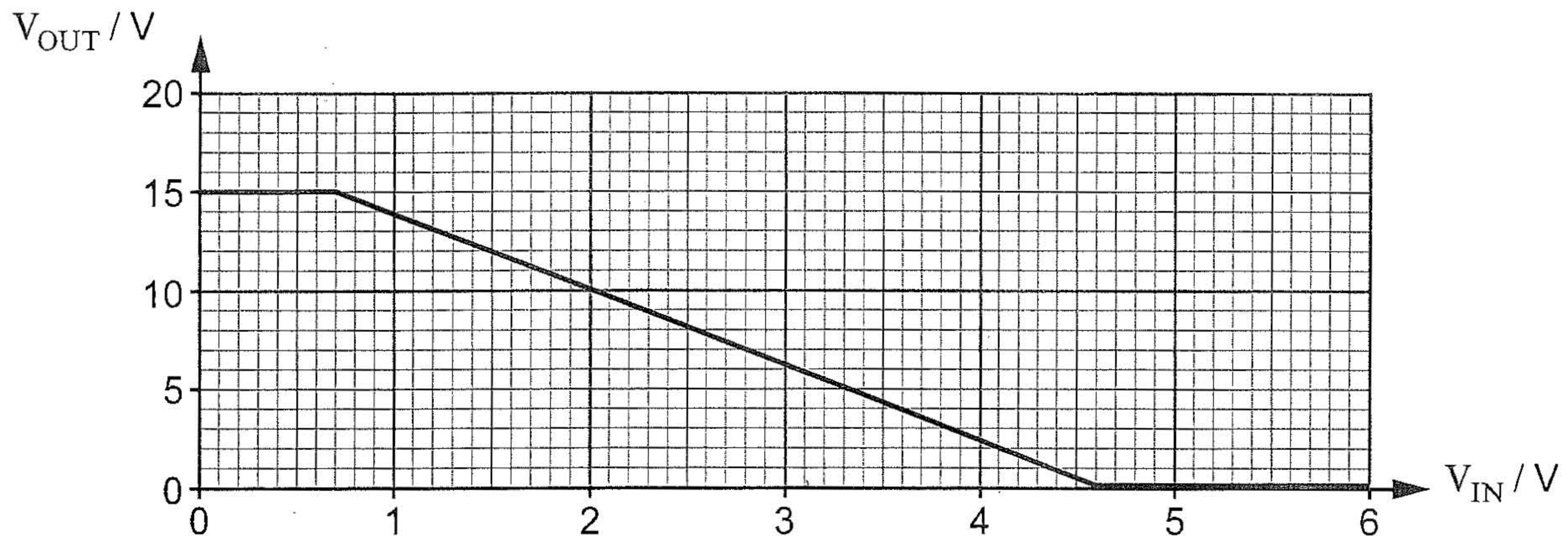- (b) A second graph was drawn to show how  $V_{OUT}$  changed as  $V_{IN}$  was increased from 0 to 6 V.



Use the graph to determine:

- (i) the minimum value of  $V_{IN}$  required to saturate the transistor;

4.6 V

[1]

- (ii) the value of  $V_{OUT}$ , when  $V_{IN} = 3.1 \text{ V}$ .

6 V

[1]

- (c)  $V_{IN} = 3.1 \text{ V}$  and the load resistor =  $120 \Omega$ .

Calculate the collector current and the power dissipated in the transistor. [3]

$$P = VI$$


$$I = \frac{V}{R} = \frac{3.1}{120} = 0.02583 \text{ A}$$

$$0.08 \text{ W} = 3.1 \times 0.02583$$

$$I_C = \frac{15}{120} = 0.125$$


**TURN OVER FOR THE LAST QUESTION.**



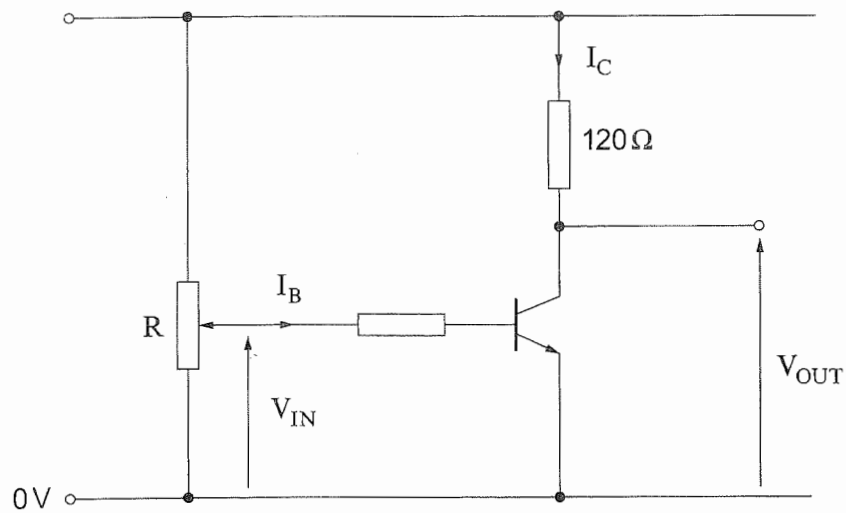

Potentiometer  $R$  is varied and readings of  $V_{IN}$ ,  $V_{OUT}$ ,  $I_B$  and  $I_C$  are taken.

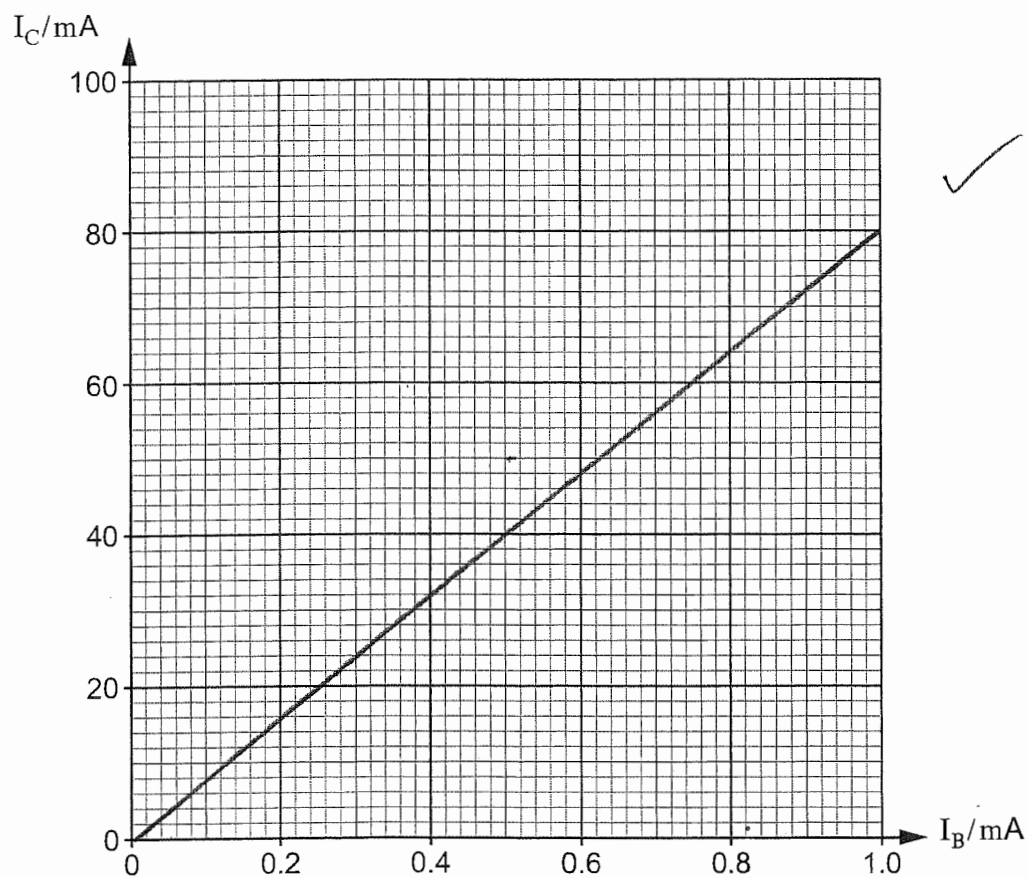- (a) As the base current is increased from 0.2 to 0.8 mA the collector current increases from 16 to 64 mA and the transistor does not saturate.
- (i) Complete the graph below to show how the ammeter readings change as  $I_B$  is increased from 0 to 1 mA. The transistor does not saturate. [1]




- (ii) Determine the current gain ( $h_{FE}$ ) of the transistor.

[1]

Examiner only

$$h_{FE} = \frac{I_C}{I_B} = \frac{0.8 \text{ mA}}{64 \text{ mA}} = 0.0125$$

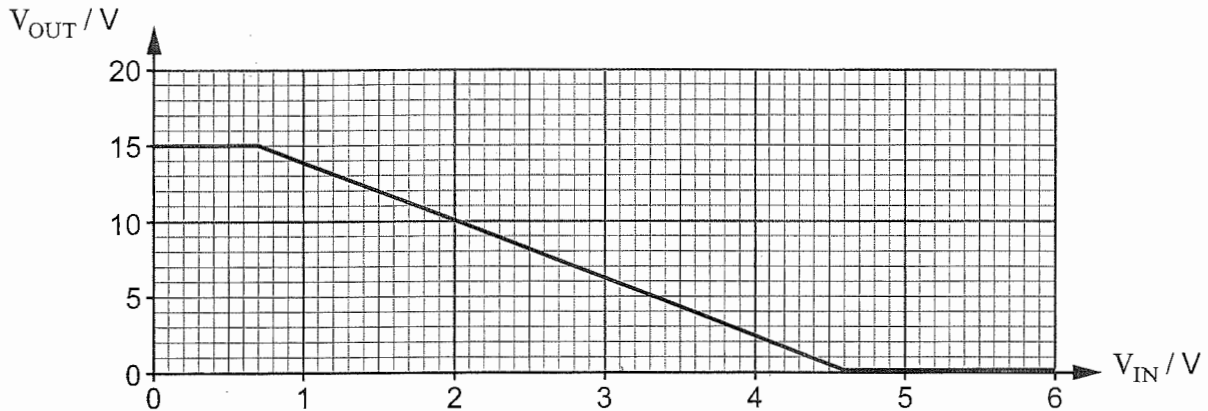- (b) A second graph was drawn to show how  $V_{OUT}$  changed as  $V_{IN}$  was increased from 0 to 6V.



Use the graph to determine:

- (i) the minimum value of  $V_{IN}$  required to saturate the transistor;

4.5V

[1]

- (ii) the value of  $V_{OUT}$ , when  $V_{IN} = 3.1V$ .

6V

[1]

- (c)  $V_{IN} = 3.1V$  and the load resistor =  $120\Omega$ .

Calculate the collector current and the power dissipated in the transistor.

[3]

$$P = VI$$


$$0.08W = 3.1 \times 0.02583$$

$$I = \frac{V}{R} = \frac{3.1}{120} = 0.02583A$$

$$I_C = \frac{15}{120} = 0.125A$$

**TURN OVER FOR THE LAST QUESTION.**

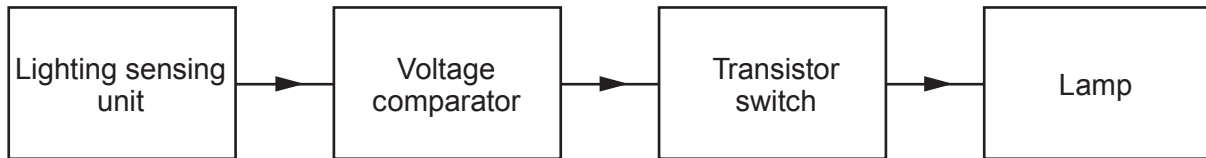9. A system is required to turn on a 12V, 2A lamp automatically at night.




The specification for the system is:

- the system requires a 12V power supply;
- the light level at which the lamp comes on should be adjustable;
- the lamp is capable of being driven directly from the transistor switch output;
- the voltage comparator reference voltage is 3V.

Complete the circuit diagram for the system by adding:

- the component values required to provide a reference voltage,  $V_{REF} = 3V$ ;
- the light sensing sub-system;
- a facility for adjusting the light level at which the lamp comes on;
- the transistor switch;
- the output sub-system.


[7]

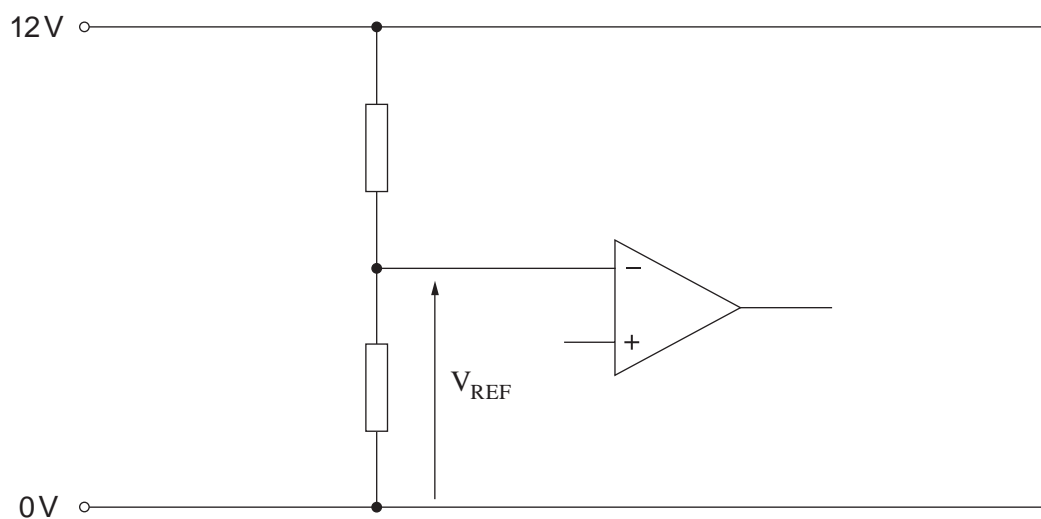

**END OF PAPER**



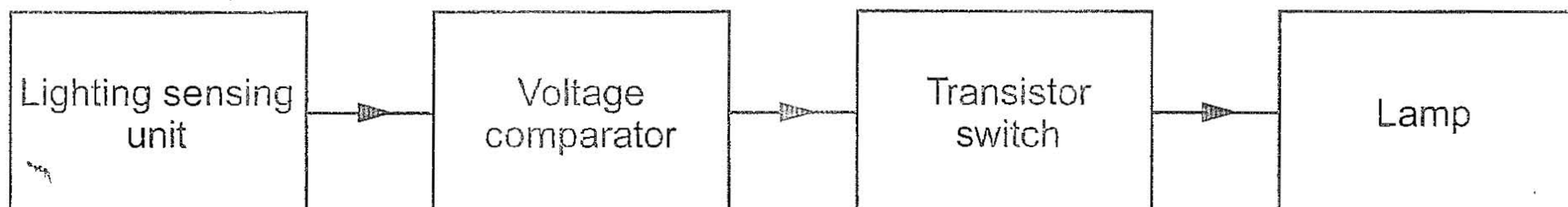9. A system is required to turn on a 12V, 2A lamp automatically at night.




The specification for the system is:

- the system requires a 12V power supply;
- the light level at which the lamp comes on should be adjustable;
- the lamp is capable of being driven directly from the transistor switch output;
- the voltage comparator reference voltage is 3V.

Complete the circuit diagram for the system by adding:


- the component values required to provide a reference voltage,  $V_{REF} = 3V$ ;
- the light sensing sub-system;
- a facility for adjusting the light level at which the lamp comes on;
- the transistor switch;
- the output sub-system.

[7]

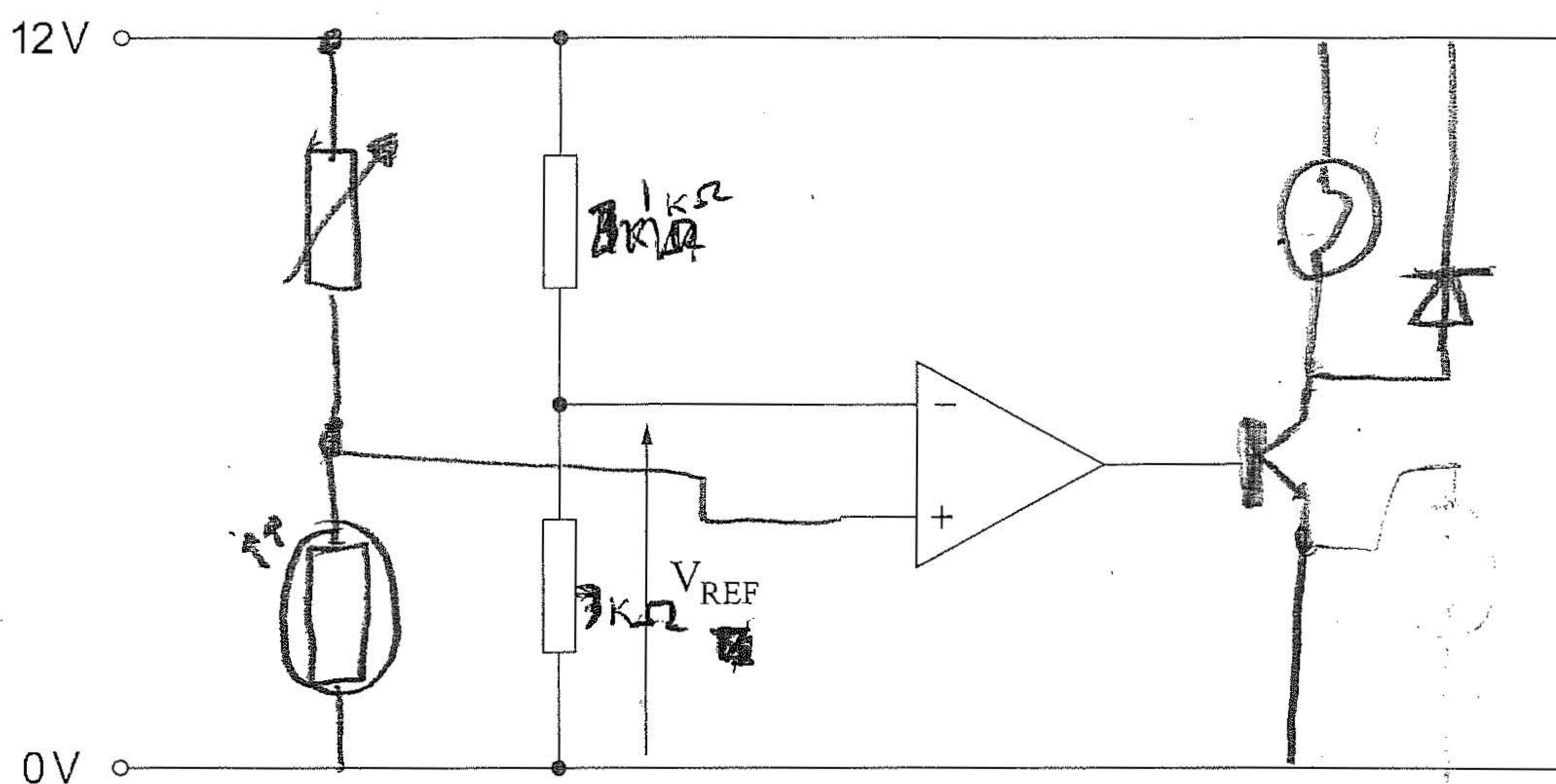

END OF PAPER

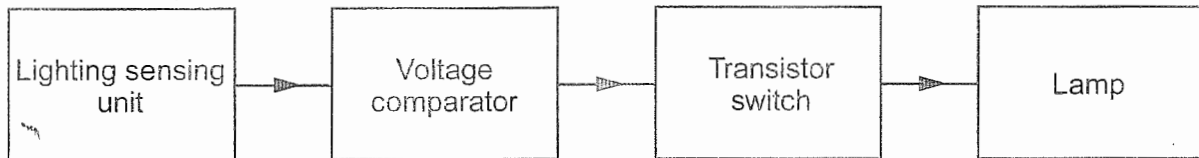9. A system is required to turn on a 12V, 2A lamp automatically at night.




The specification for the system is:

- the system requires a 12V power supply;
- the light level at which the lamp comes on should be adjustable;
- the lamp is capable of being driven directly from the transistor switch output;
- the voltage comparator reference voltage is 3V.

Complete the circuit diagram for the system by adding:


- the component values required to provide a reference voltage,  $V_{REF} = 3V$ ;
- the light sensing sub-system;
- a facility for adjusting the light level at which the lamp comes on;
- the transistor switch;
- the output sub-system.

[7] 6

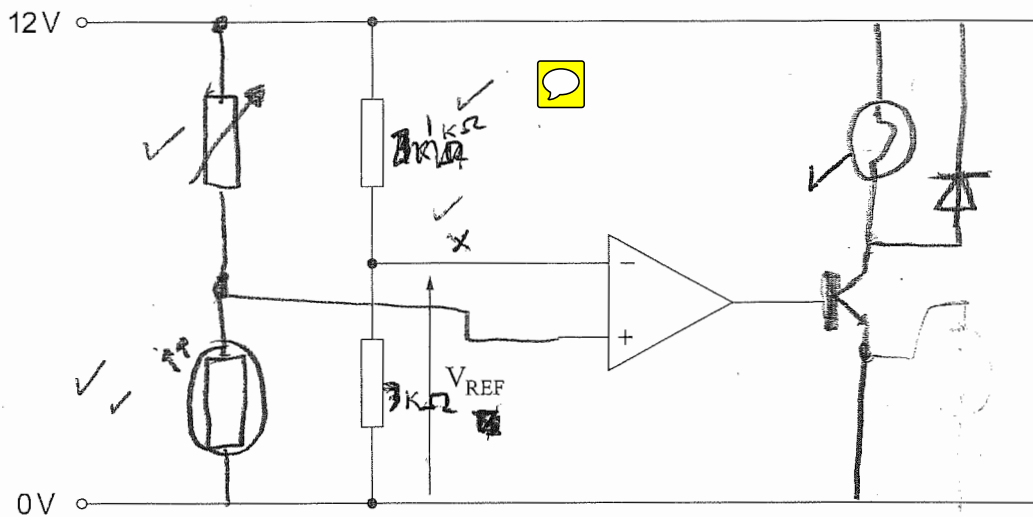

END OF PAPER

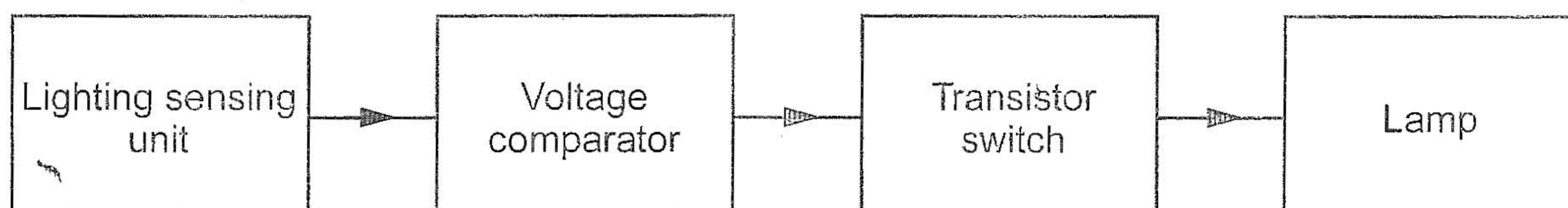9. A system is required to turn on a 12V, 2A lamp automatically at night.




The specification for the system is:

- the system requires a 12V power supply;
- the light level at which the lamp comes on should be adjustable;
- the lamp is capable of being driven directly from the transistor switch output;
- the voltage comparator reference voltage is 3V.

Complete the circuit diagram for the system by adding:

- the component values required to provide a reference voltage,  $V_{REF} = 3V$ ;
- the light sensing sub-system;
- a facility for adjusting the light level at which the lamp comes on;
- the transistor switch;
- the output sub-system.


[7]

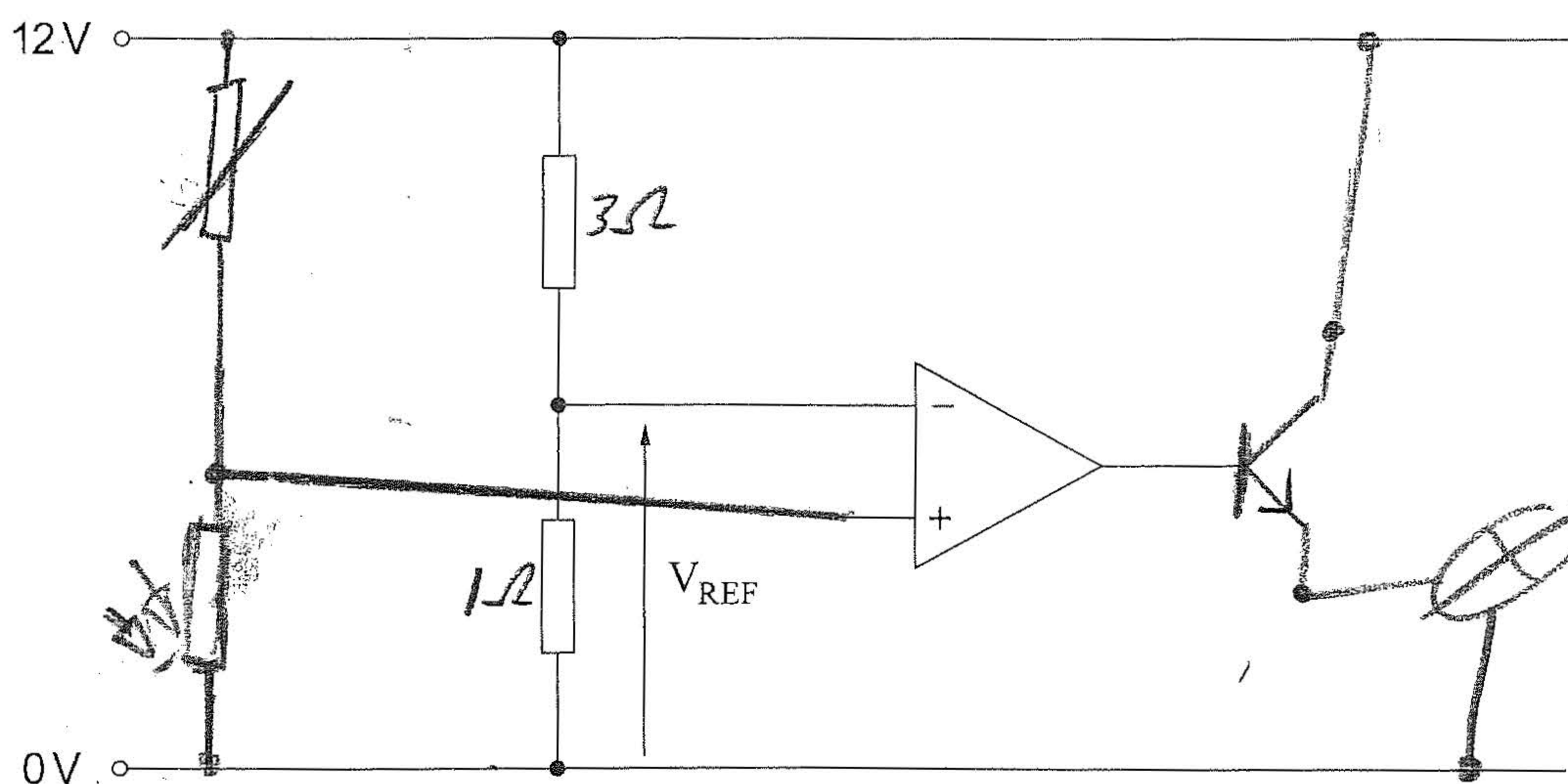

END OF PAPER



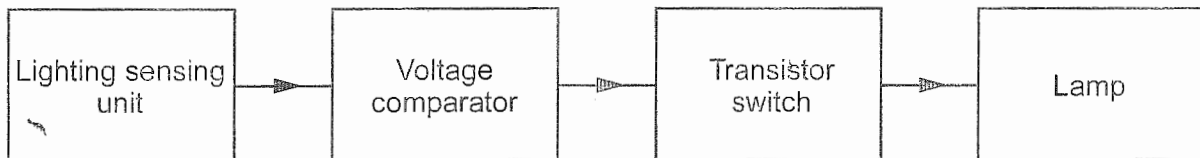9. A system is required to turn on a 12V, 2A lamp automatically at night.




The specification for the system is:

- the system requires a 12V power supply;
- the light level at which the lamp comes on should be adjustable;
- the lamp is capable of being driven directly from the transistor switch output;
- the voltage comparator reference voltage is 3V.

Complete the circuit diagram for the system by adding:


- the component values required to provide a reference voltage,  $V_{REF} = 3V$ ;
- the light sensing sub-system;
- a facility for adjusting the light level at which the lamp comes on;
- the transistor switch;
- the output sub-system.

[7] 5

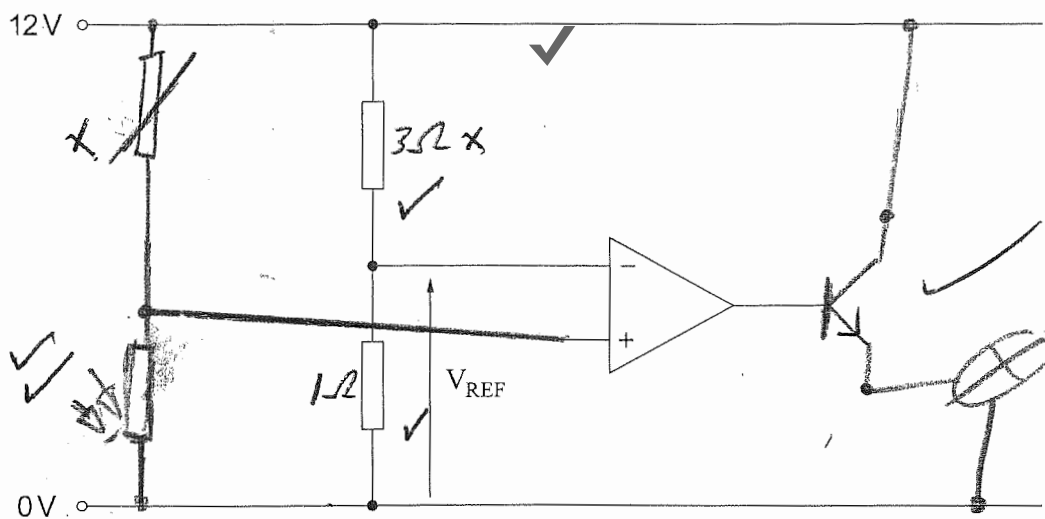

END OF PAPER

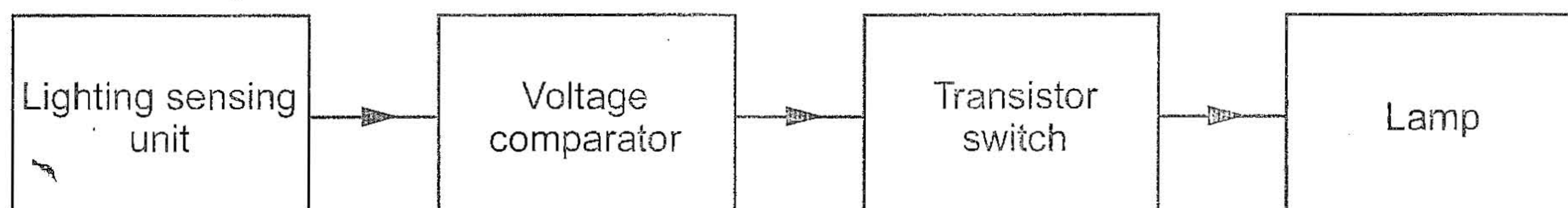9. A system is required to turn on a 12 V, 2 A lamp automatically at night.




The specification for the system is:

- the system requires a 12 V power supply;
- the light level at which the lamp comes on should be adjustable;
- the lamp is capable of being driven directly from the transistor switch output;
- the voltage comparator reference voltage is 3 V.

Complete the circuit diagram for the system by adding:

- the component values required to provide a reference voltage,  $V_{REF} = 3\text{ V}$ ;
- the light sensing sub-system;
- a facility for adjusting the light level at which the lamp comes on;
- the transistor switch;
- the output sub-system.


[7]

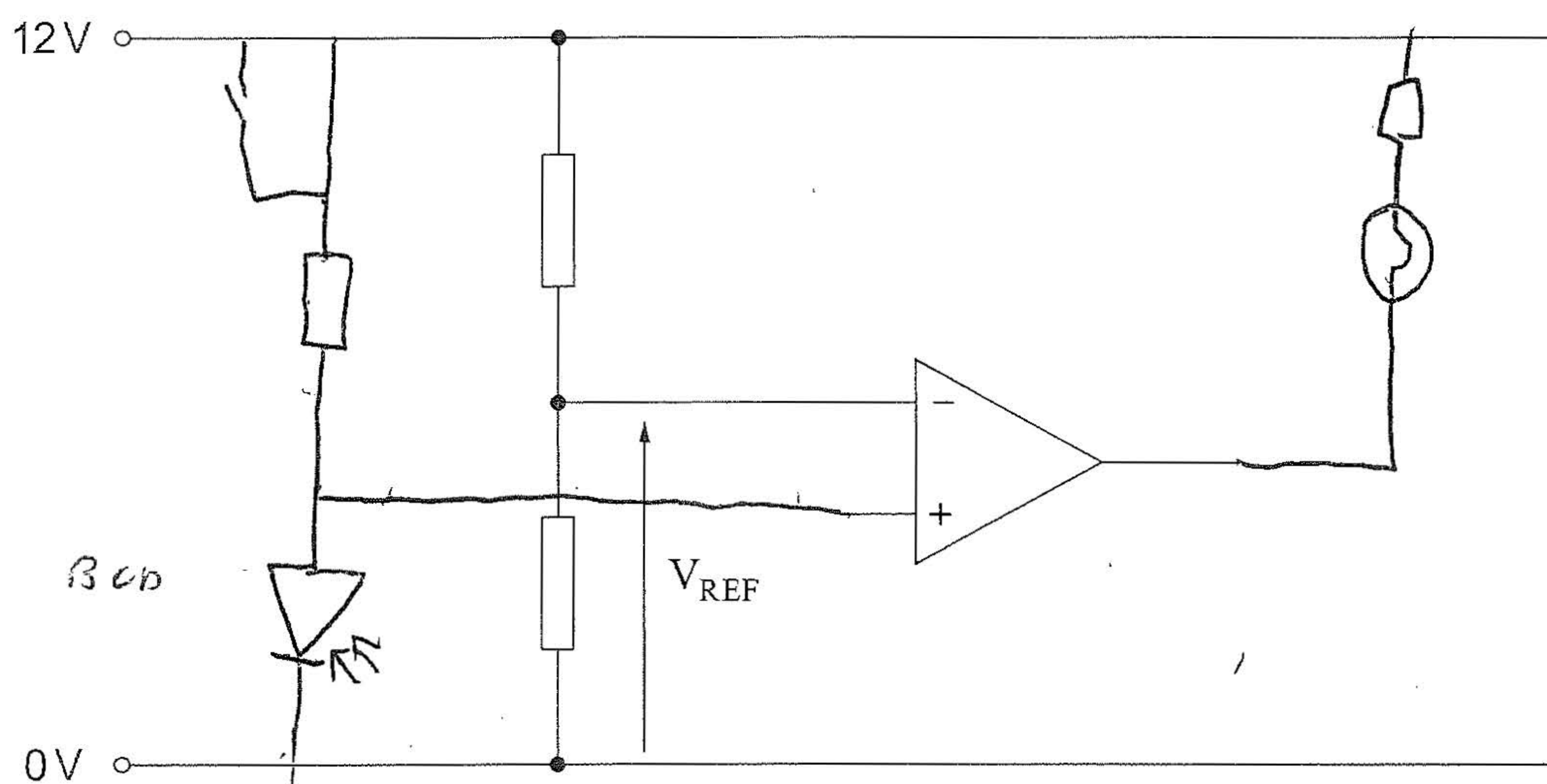

**END OF PAPER**



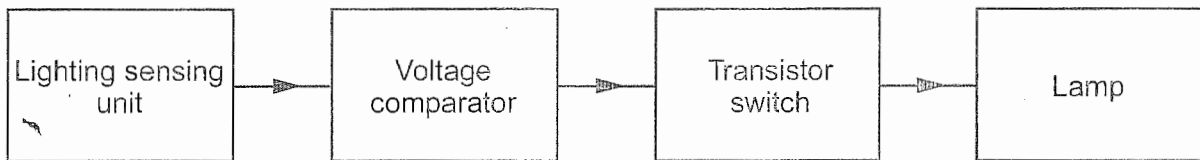9. A system is required to turn on a 12V, 2A lamp automatically at night.




The specification for the system is:

- the system requires a 12V power supply;
- the light level at which the lamp comes on should be adjustable;
- the lamp is capable of being driven directly from the transistor switch output;
- the voltage comparator reference voltage is 3V.

Complete the circuit diagram for the system by adding:

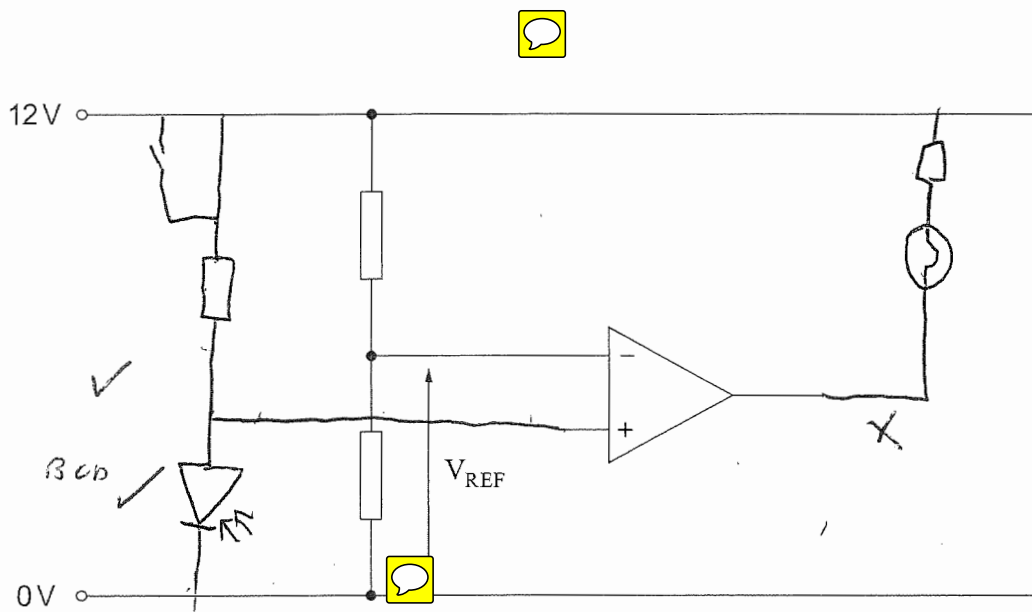- the component values required to provide a reference voltage,  $V_{REF} = 3V$ ;
- the light sensing sub-system;
- a facility for adjusting the light level at which the lamp comes on;
- the transistor switch;
- the output sub-system.



END OF PAPER